

Fall 2018



California State University, Northridge  
Department of Electrical & Computer Engineering

Experiment 8  
Operational Amplifiers  
November 5, 2018

ECE 240L  
Professor: Franco Mikhailidis

Group 2  
Author: Ridge Tejuco  
Lab partner: Jonathan Roa

### Introduction:

The purpose of this experiment is to understand how to analyze circuits that contain operational amplifiers, through modeling them as an ideal, using their properties to simplify a circuit, and determining their outputs. Through this experiment, the different types of output voltages possible from an operational amplifier will be observed.

### Equipment used:

Type	Model	Serial No.	Calibration Date
Function Generator	Agilent 33220A	MY44017172	N/A
Oscilloscope	Tektronix 2213A	LR37158	N/A
Digital Multimeter	Tektronix CDM250	CDM-250TW5238 0	N/A
DC power supply	Agilent E3630	MY40004246	N/A

### Parts Used:

QTY	Component	Value	Tolerance	Type
1	Resistor	3.3kΩ	+/- 5%	Carbon
1	Resistor	10kΩ	+/- 5%	Carbon
1	Resistor	6.2kΩ	+/- 5%	Carbon
1	Resistor	27kΩ	+/- 5%	Carbon
1	Resistor	4.7kΩ	+/- 5%	Carbon
1	Resistor	100kΩ	+/- 5%	Carbon

### Software Used:

1. Google Docs
2. Krita
3. Snipping Tool
4. Pspice

### Theory:

An Op. Amp. takes 2 input voltages and applies a gain  $A_V$  between the difference of inputs  $V_A$  and  $V_B$  as shown in figure 8.1

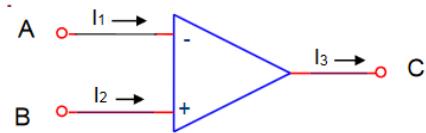


Figure 8.1

The important characteristics of an ideal op amp are that it has an infinite gain and infinite resistance which results in the following properties.

The difference in voltages between inputs A and B are 0.

$$V_A - V_B = 0\text{V} \quad \text{or} \quad V_A = V_B$$

There is no current that travels through the inputs.

$$I_1 = I_2 = 0\text{A}$$

The output current is not 0.

Operational amplifiers come in the form of a DIP integrated circuit shown in Figure 8.5

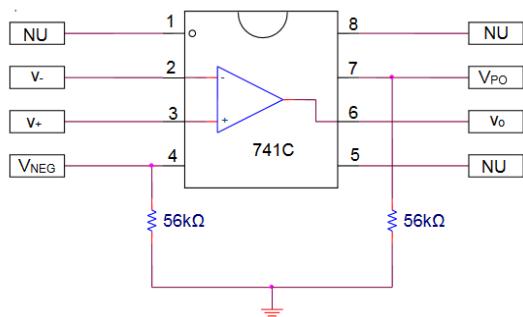


Figure 8.5

Pin 2 is the inverting input. Pin 3 is the non-inverting input. Pin 4 is the negative power. Pin 6 is the output of the Op amp, and Pin 7 is the positive power.

Procedure & Results:

1. The output voltage  $V_o$  of Figure 8.2 was found to be a function of  $R_F$  and  $V_i$ .

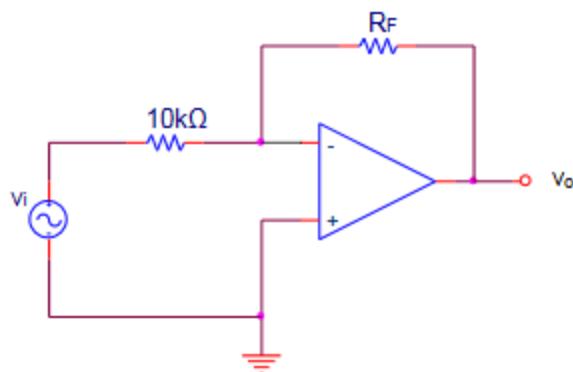


Figure 8.2

$$i = \frac{V_i}{10k\Omega} = \frac{0 - V_o}{R_F}$$


$$V_o = -I_1 R_F = -V_i \left( \frac{R_F}{10k\Omega} \right)$$

Figure 8.2 was constructed for values of  $R_F$  as  $10k\Omega$ ,  $27k\Omega$ ,  $100k\Omega$


$V_o$ ,  $A_v$ , and % error of  $A_v$  were recorded with an for an amplitude of .3v in Table 8.1

Table 8.2	Measured			Calculated			
	$R_F$	$V_i$	$V_o$	$A_v$	$V_i$	$V_o$	$A_v$
$10k\Omega$	0.30 v	-0.29 v	-9.84	0.30v	-30 v	-1.0	1.6%
$27k\Omega$	0.30 v	-0.80 v	-2.667	0.30v	-0.81	-2.7	1.2%
$100k\Omega$	0.30	-2.91	--9.7	0.30v	-3.0v	-10.0	3%


Figure 8.2 was simulated in Pspice 8.2 and the results were shown in graph 8.2a-c

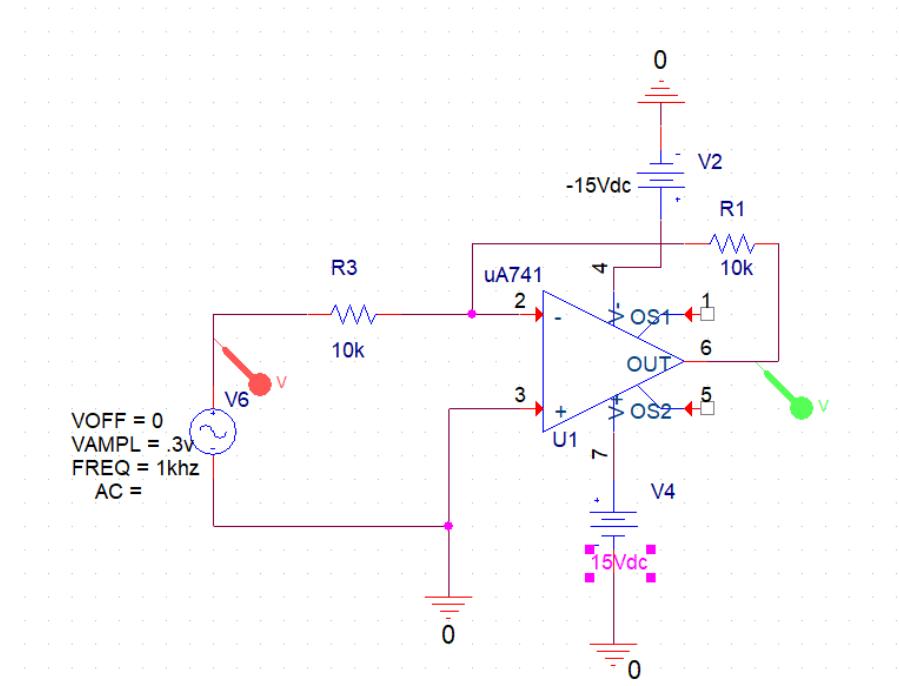


(Pspice 8.2)

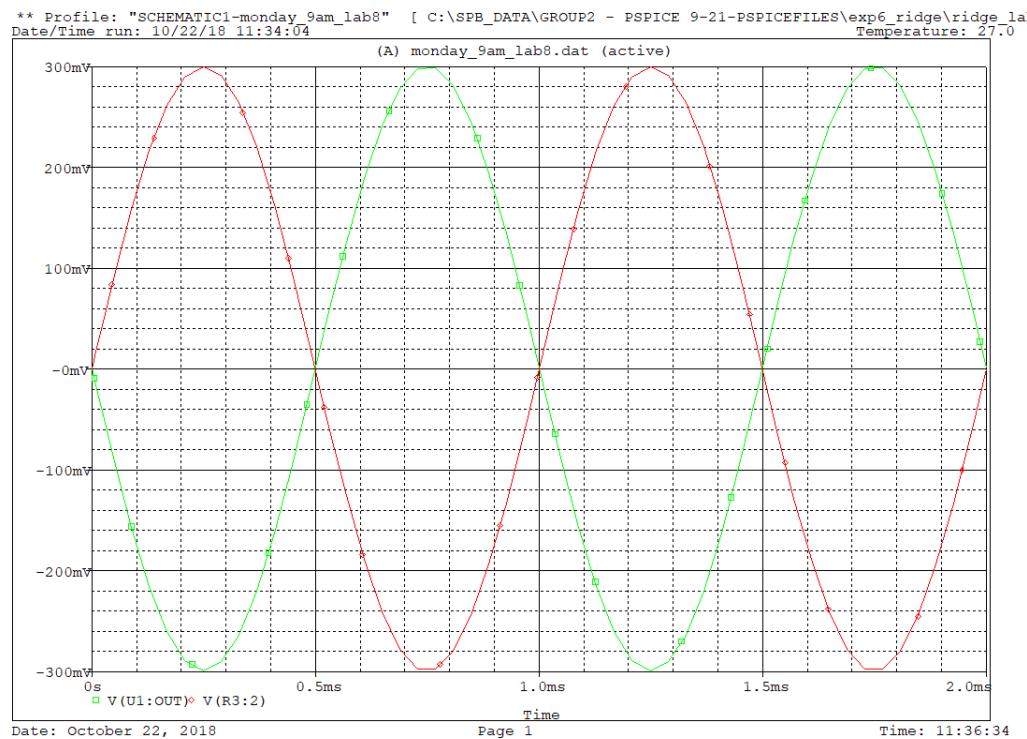

Graph 8.2a

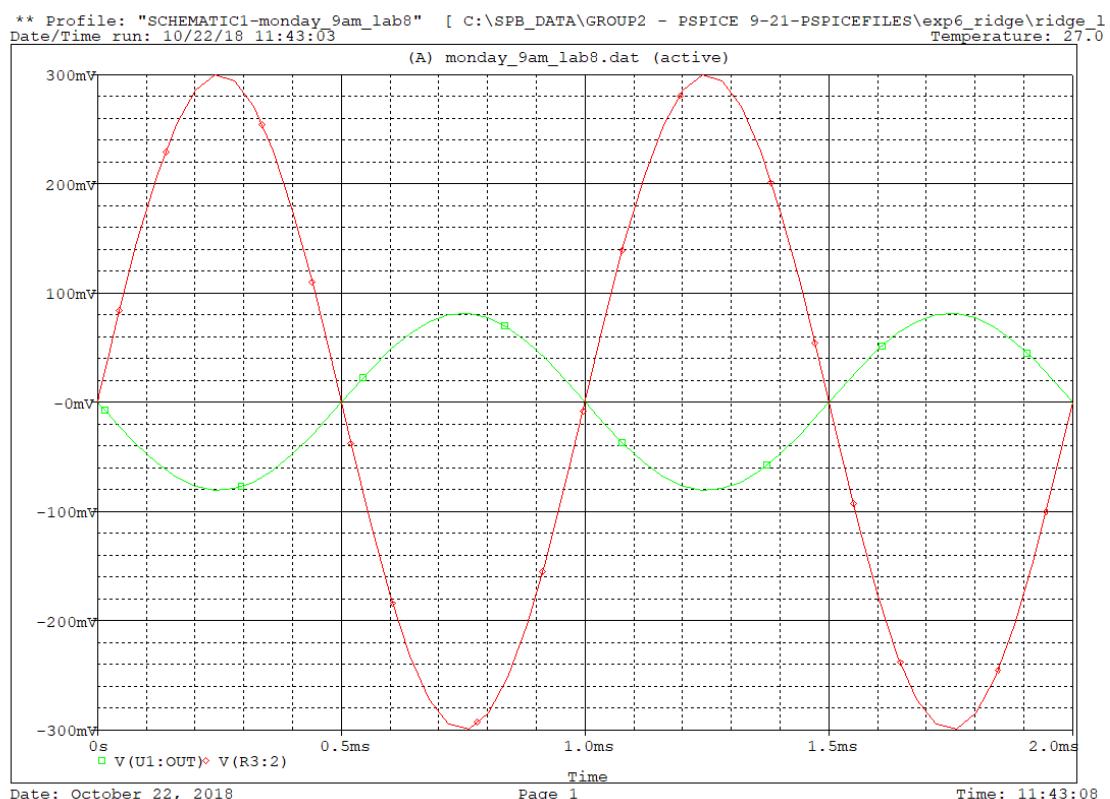


Graph 8.2b

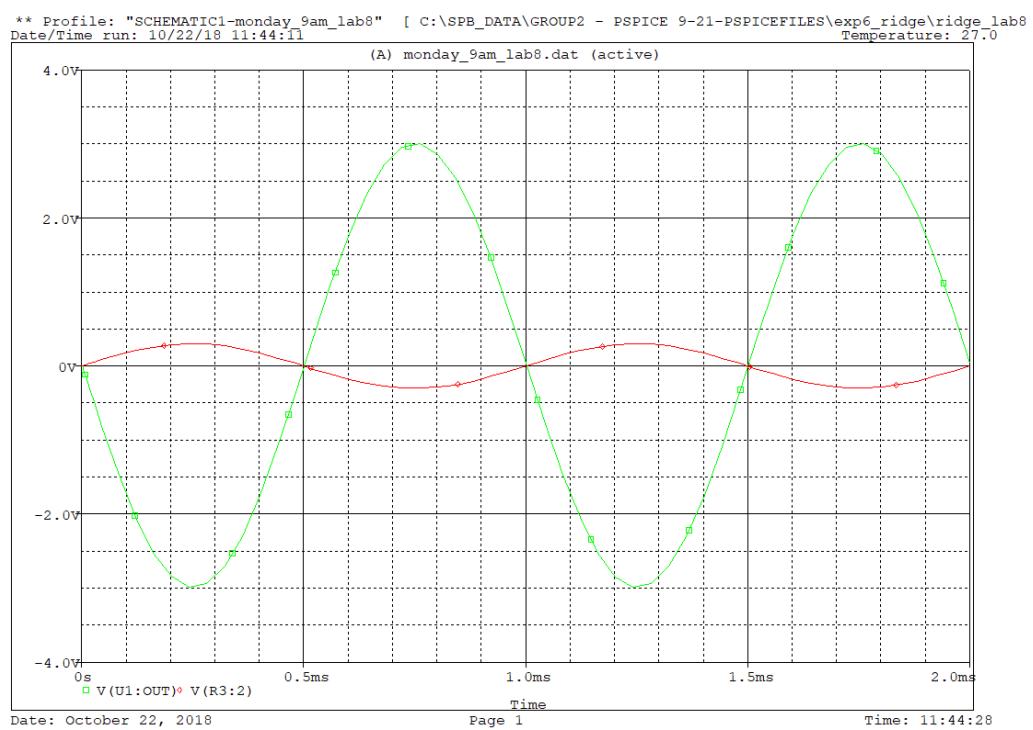

Graph 8.2c

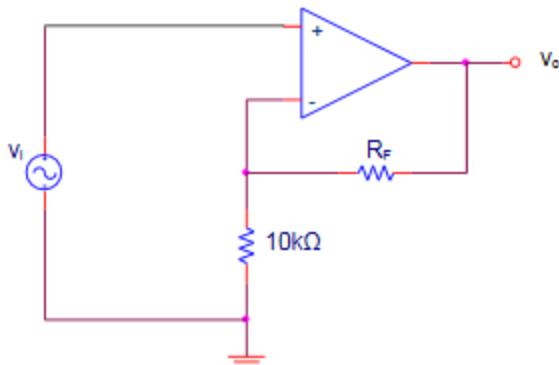2. The output voltage  $V_o$  of Figure 8.3 was found to be a function of  $R_F$  and  $V_i$ .



$$I = \frac{V_i}{10k\Omega} \quad V_o = V_i - (-R_F)$$



$$V_o = V_i + V_i \left( \frac{R_F}{10k\Omega} \right)$$

$$V_o = V_i \left( 1 + \frac{R_F}{10k\Omega} \right)$$


Figure 8.3

Figure 8.3 was constructed with values of  $R_F$  as  $10k\Omega$ ,  $27k\Omega$ , and  $100k\Omega$ .


An oscilloscope was used to measure  $V_i$  and  $V_o$ . The results were displayed in Pictures 8.3a-d  
(Picture 8.3a) (Picture 8.3b)

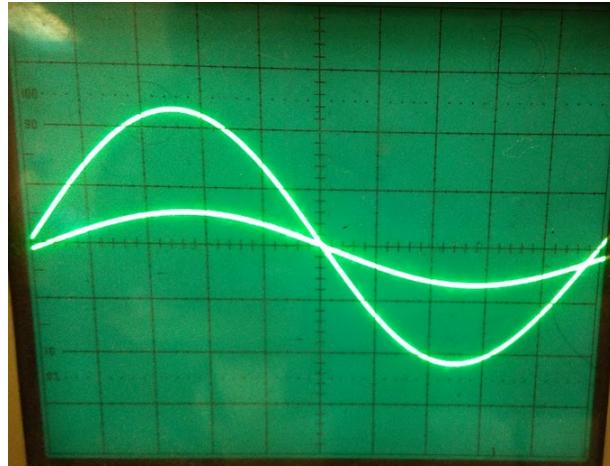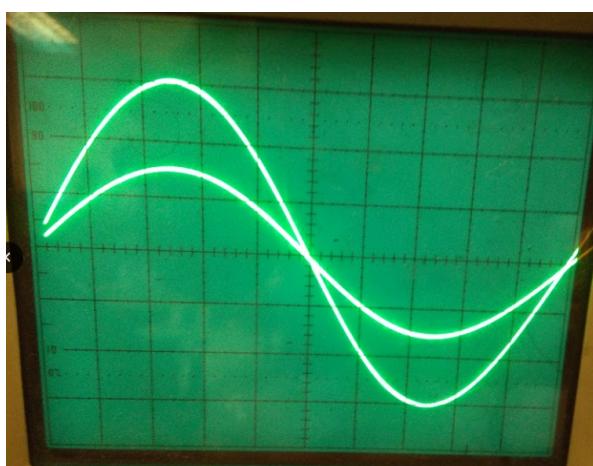

(Picture 8.3c)

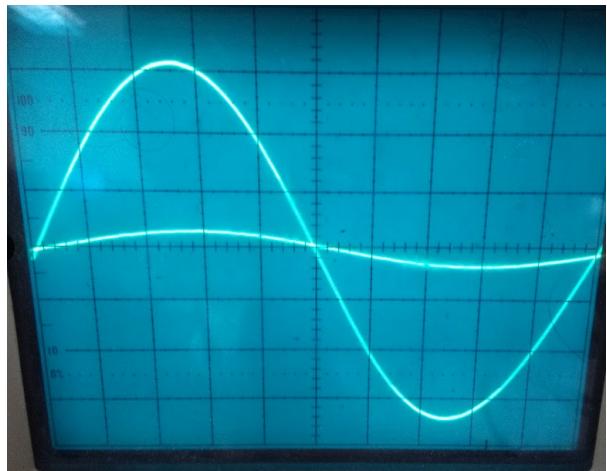


(Picture 8.3d)

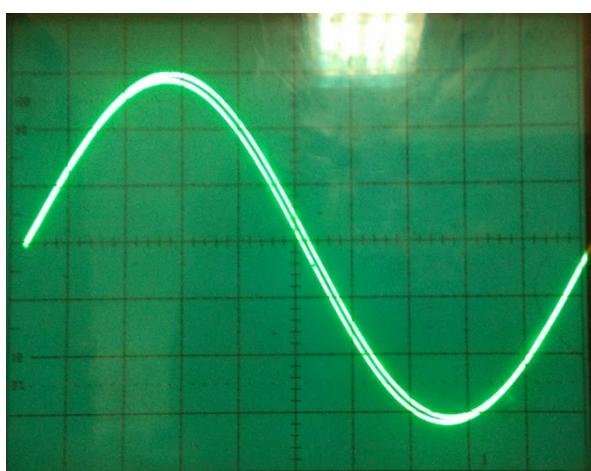


$V_O$ ,  $A_V$ , and  $A_V\%$  error were recorded with in Table 8.3

Table 8.3	Measured			Calculated			
	$R_F$	$V_I$	$V_O$	$A_V$	$V_I$	$V_O$	$A_V$
10k $\Omega$	0.30v	0.605 v	2.017	0.30v	.60v	2.0	.85%
27k $\Omega$	0.30v	1.150 v	3.83	0.30v	1.11v	3.7	3.5%
100k $\Omega$	0.30v	3.250 v	10.8	0.30v	3.3v	11.0	1.82%
Shorted	.30v	0.295 v	1.02	0.30v	.30v	1.0	2.0%


The circuit was then simulated in pspice 8.3 and results shown in graph 8.3a -d

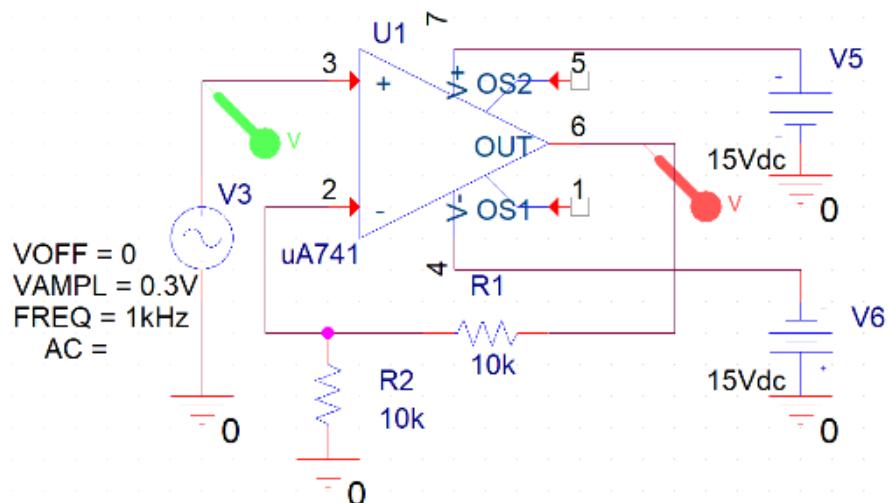


(Pspice 8.3)

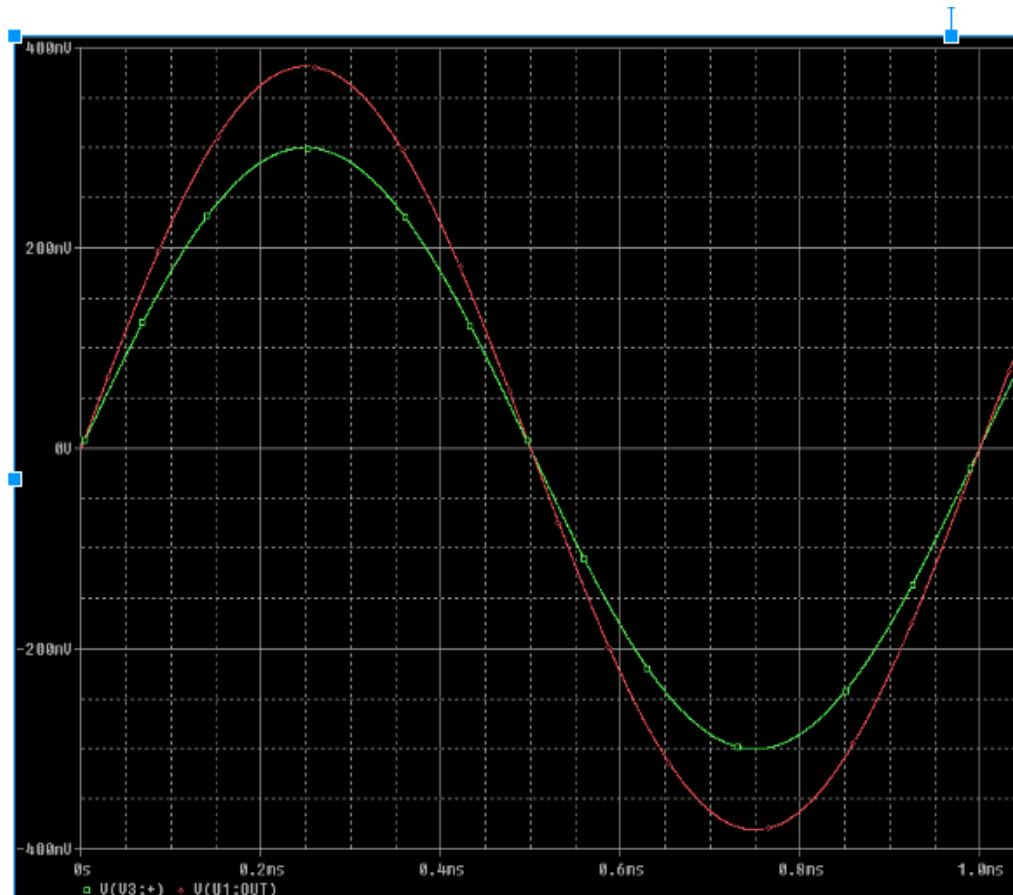

Graph 8.3a

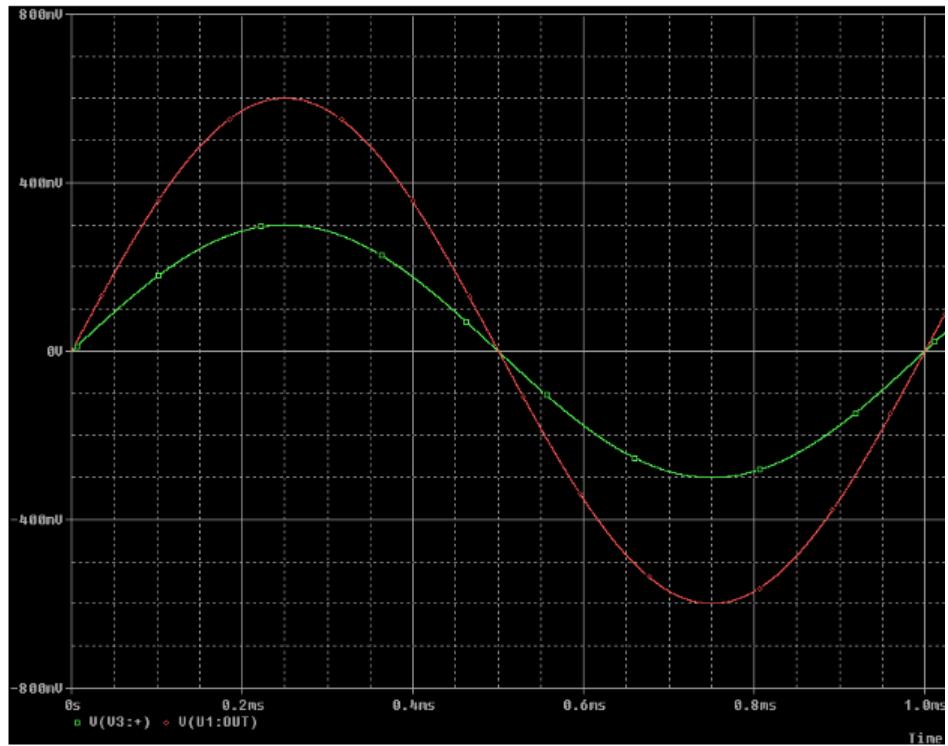

Graph 8.3b

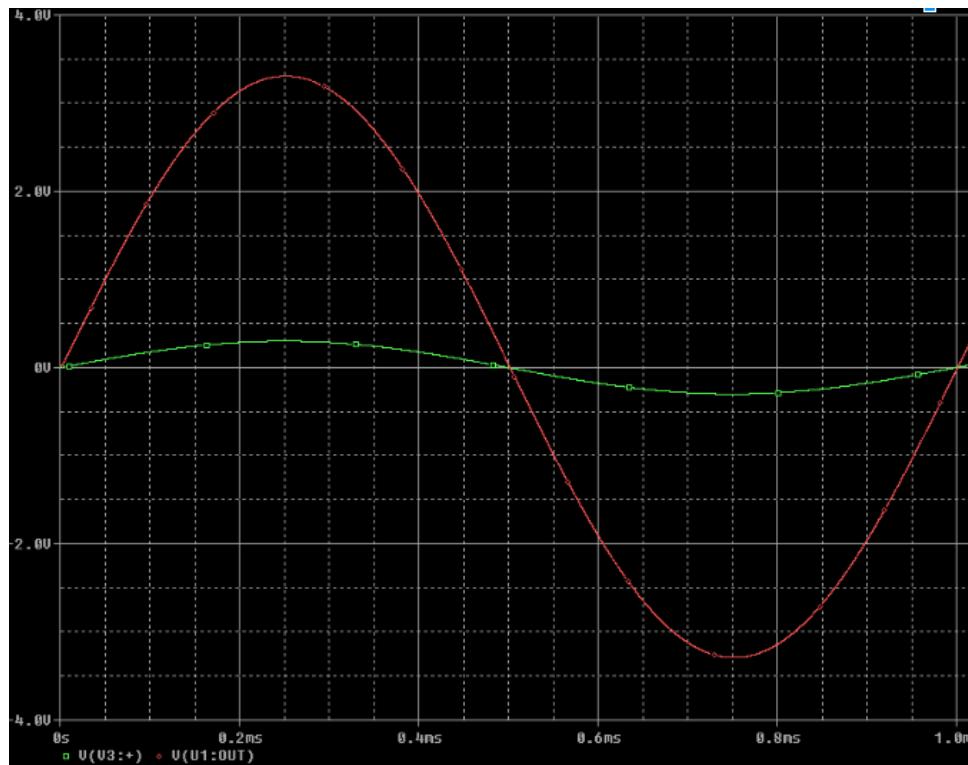

Graph 8.3c

3. The output voltage  $V_o$  of Figure 8.4 was found to be a function of  $R_F$  and  $V_i$ .

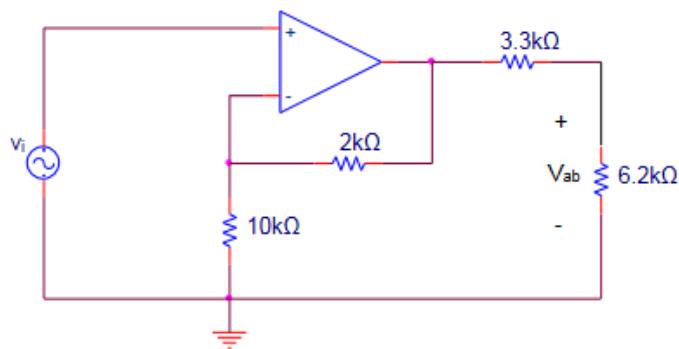


Figure 8.4

$$I_1 = \frac{V_i}{10k\Omega}$$

$$V_o = V_i \left(1 + \frac{2k}{10k}\right) \quad \boxed{V_o = 1.2V_i}$$

$$I_2 = \frac{V_o}{3.3k + 6.2k}$$


$$V_{ab} = V_o \left(\frac{6.2}{6.2 + 3.3}\right) = (.6526)V_o$$

Figure 8.4 was constructed.

An oscilloscope was used to measure  $V_i$ ,  $V_o$ , and  $V_{ab}$ .

The results were displayed in Pictures 8.4a-b(Picture 8.4a)


(Picture 8.4b)

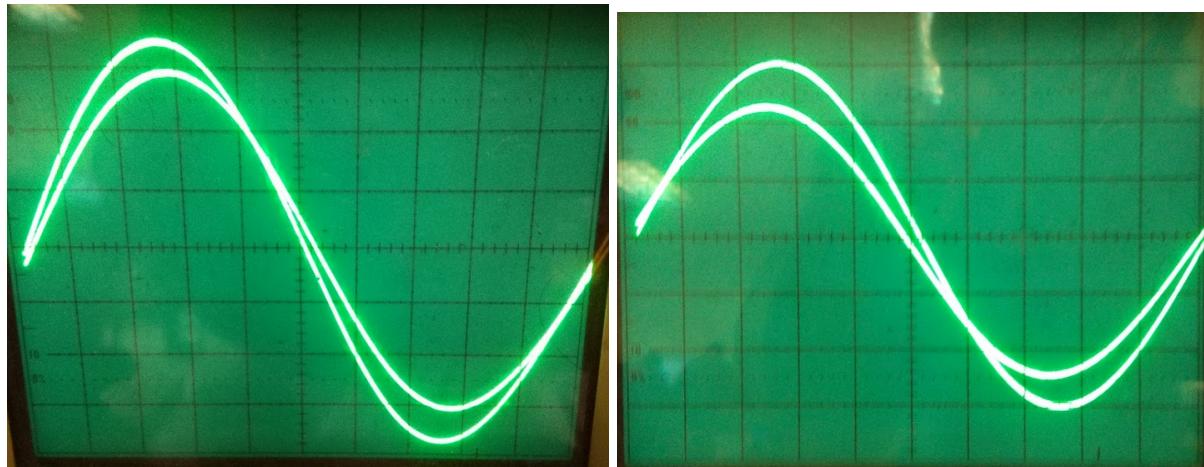


The output voltage,  $V_{ab}$ , and their gains were recorded in Table 8.4

Table 8.4	$V_o$	$A_{V1}$	$V_{ab}$	$A_{V2}$	$A_V$
Measured	0.355 v	1.18	0.230 v	0.648	0.767
Calculated	0.360 v	1.20	0.235 v	0.653	0.783
% error	1.39%	1.67%	2.12%	0.76%	2.04%

Figure 8.4 was simulated in Pspice 8.4 and the results in Graph 8.4

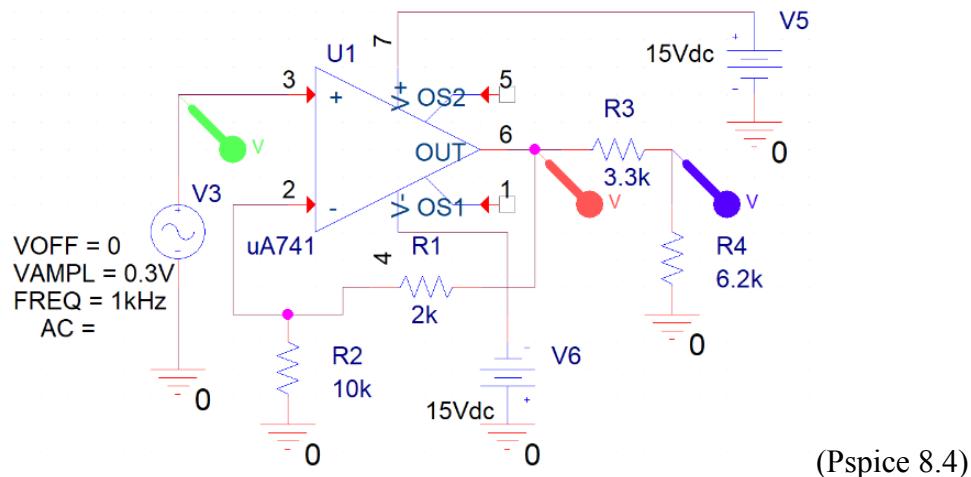

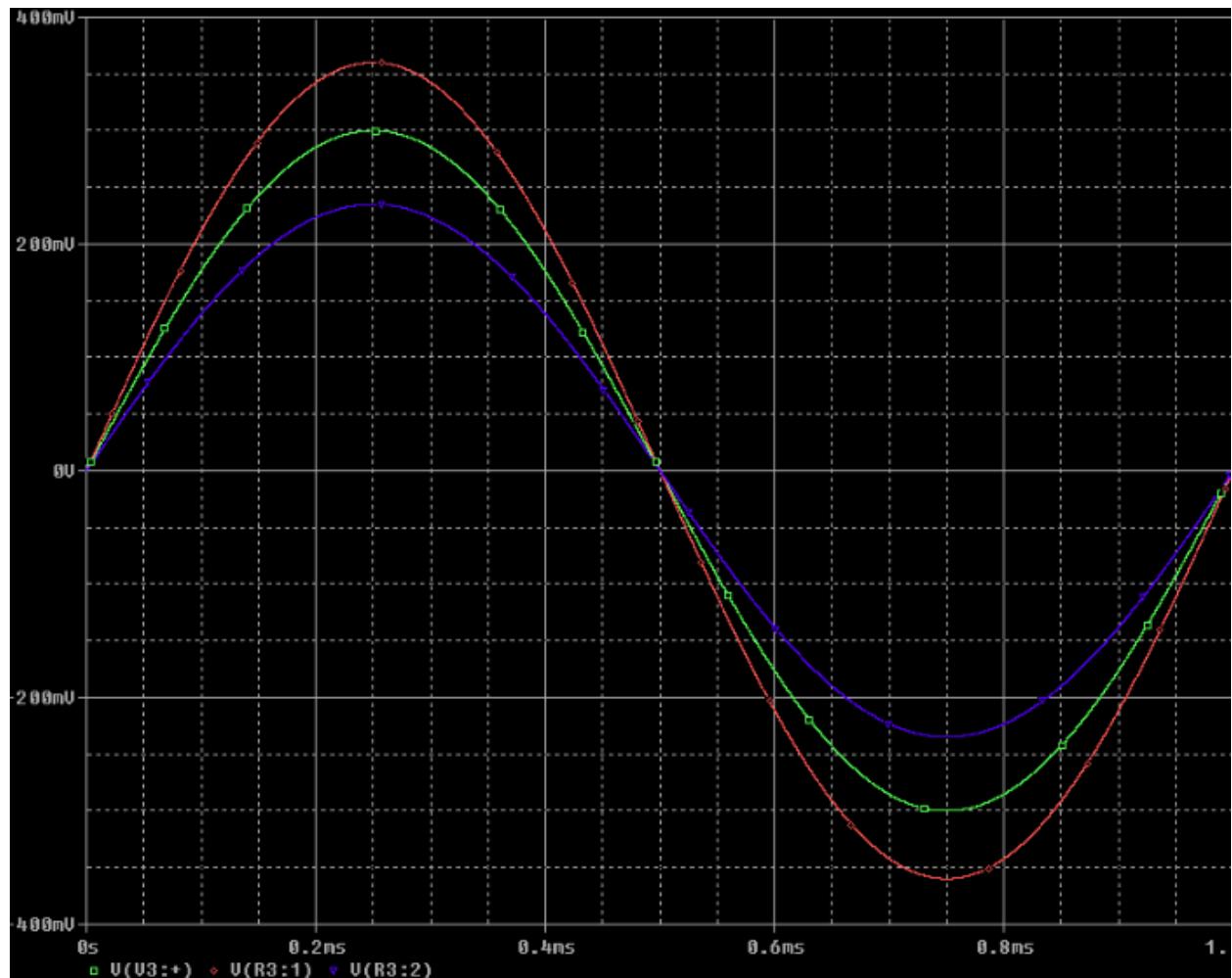

graph 8.4

### Conclusion:

The experiment was a success in the demonstration and analysis of operational amplifiers in AC circuits. In part 1 of the procedure, the inverting amplifier was successfully analyzed and built. The measured results showed minimal % error between measured and calculated gain. In part 2, the circuit was identified as a non-inverting amplifier and again the % errors were less than 5% error between the measured and calculated results. In part 3, the attenuating circuit was correctly built and analysed. In Pspice, figures 8.2, 8.3, and 8.4 were all successfully simulated and the graphs produced the exact same results as seen on the analog oscilloscope. The experiment was a success in the demonstration in the inversion , non-inversion, and attenuation of input voltages.