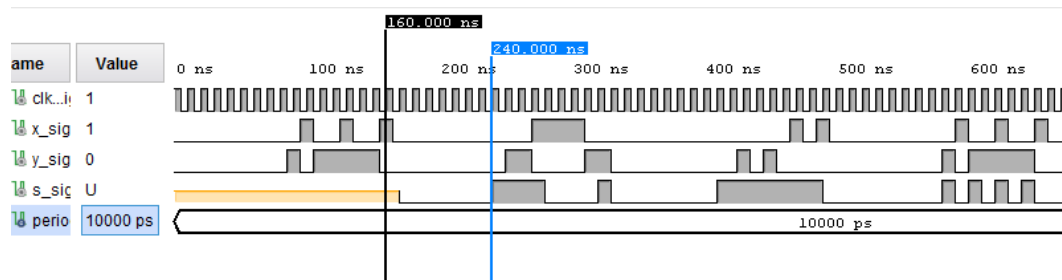


Spring 2019



Computer Assignment 3  
Professor: Shahnam Mirzaei PhD.  
Author: Ridge Tejuco  
March 24, 2019


## SA TOP RESULTS



In the test bench 3 additions take place.


The result of each bit is displayed 8 clock cycles after the x and y bit is input.

 Looking closer, the results are verified by reading s\_sig right to left.




```

0111 1101
+ 1001 0010
1 0000 1111
  
```

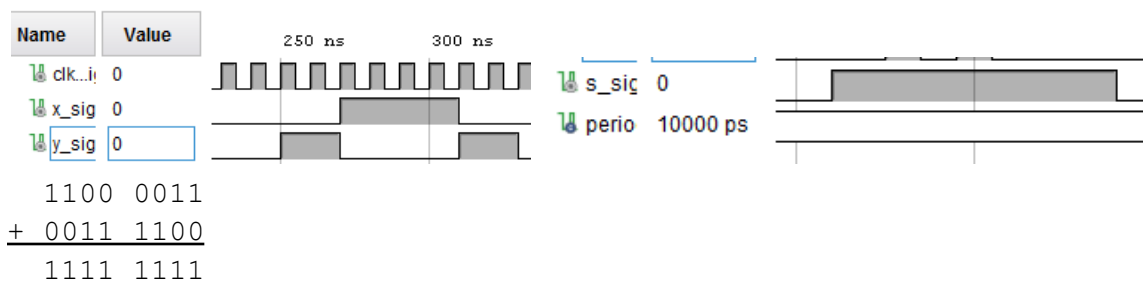

```

1100 0011
+ 0011 1100
1111 1111
  
```

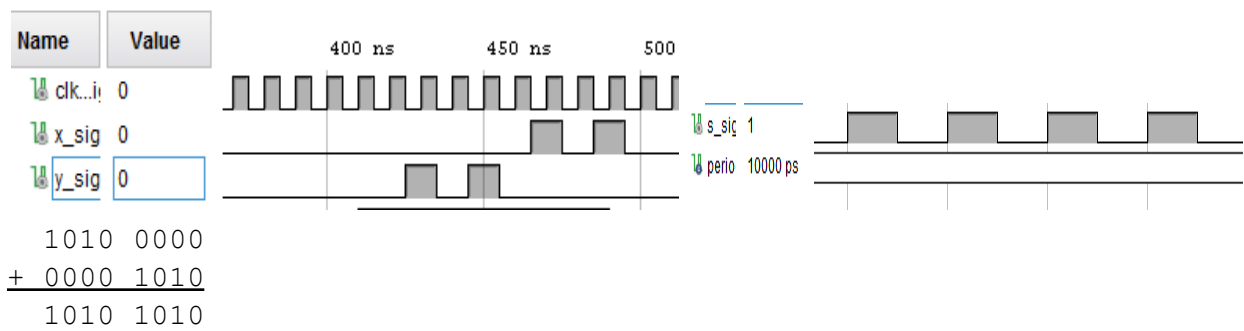

```

1010 0000
+ 0000 1010
1010 1010
  
```

```

-- sa_top.vhd
-- Ridge Tejuco
library ieee;
use ieee.std_logic_1164.all;
entity sa_top is
    port (x, y, clk: in std_logic;
          s: out std_logic);
end entity;

architecture siso of sa_top is
    signal x_out,y_out: std_logic;
    signal cout_sig, cin_sig, sum_sig: std_logic;
    signal output: std_logic;
    component shift_register_siso is
        port(clk, reset,d : IN STD_LOGIC;
              q: OUT STD_LOGIC);
    END component shift_register_siso;

    component FullAdder is
        Port ( cin,a,b : in STD_LOGIC;
              sum,cout : out STD_LOGIC);
    end component FullAdder ;

    component dff is
        port(d,clk,reset: in std_logic;
              q: out std_logic);
    end component dff;

    Begin
    X_REG: shift_register_siso
        port map(clk => clk,reset => '0',d => x,q => x_out);
    Y_REG: shift_register_siso
        port map(clk => clk,reset => '0',d => y,q => y_out);
    ADDER: FullAdder
        port map(cin => cin_sig, a => x_out,
                  b => y_out, sum => sum_sig,cout => cout_sig);
    CARRY: dff
        port map(d => cout_sig,clk => clk,reset => '0',q =>
cin_sig);
    SUM_REG: shift_register_siso
        port map(clk => clk,reset => '0',d => sum_sig,q =>
output);
        s <= output;
    end siso;

```

```

--sa_top_tb.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity sa_top_tb is
-- Port ( );
end sa_top_tb;
architecture Behavioral of sa_top_tb is
    signal clk_sig: std_logic := '0';
    signal x_sig,y_sig,s_sig: std_logic;
    constant period: time := 10ns;
    component sa_top
    port (x, y, clk: in std_logic;
    s: out std_logic);
    end component;
    begin
    UUT: sa_top
        port map(x => x_sig,y => y_sig,clk => clk_sig,s => s_sig);
    clock: process
        begin
            clk_sig <= not clk_sig;
            wait for period/2;
        end process;
    STIM: process
        begin
            x_sig <= '0'; y_sig <= '0';
            wait for period/2;
            wait for period*8;
-- next 8 periods is (0111 1101 + 1001 0010) = 1 0000 1111
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '1';y_sig <= '0'; wait for period;
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '1';y_sig <= '1'; wait for period;
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '1';y_sig <= '0'; wait for period;
            x_sig <= '0'; y_sig <= '0';
            wait for period*8;
            wait for period/2;
-- next 8 periods is (0011 1100 + 1100 0011) = 1111 1111
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '0';y_sig <= '1'; wait for period;
            x_sig <= '1';y_sig <= '0'; wait for period;
            x_sig <= '1';y_sig <= '0'; wait for period;
            x_sig <= '1';y_sig <= '0'; wait for period;

```

```

        x_sig <= '1'; y_sig <= '0'; wait for period;
        x_sig <= '0'; y_sig <= '1'; wait for period;
        x_sig <= '0'; y_sig <= '1'; wait for period;

        x_sig <= '0'; y_sig <= '0';
        wait for period*8;
        wait for period/2;
-- next 8 periods is (1010 0000 + 0000 1010) = 1010 1010
        x_sig <= '0'; y_sig <= '0'; wait for period;
        x_sig <= '0'; y_sig <= '1'; wait for period;
        x_sig <= '0'; y_sig <= '0'; wait for period;
        x_sig <= '0'; y_sig <= '1'; wait for period;
        x_sig <= '0'; y_sig <= '0'; wait for period;
        x_sig <= '1'; y_sig <= '0'; wait for period;
        x_sig <= '0'; y_sig <= '0'; wait for period;
        x_sig <= '1'; y_sig <= '0'; wait for period;
    end process;
end Behavioral;

```

```

-- shift_register_asis.vhd
-- Ridge Tejuco
library ieee;
use ieee.std_logic_1164.ALL;
entity shift_register_asis is
    port(      clk, reset,d : IN STD_LOGIC;
           q: OUT STD_LOGIC);
END shift_register_asis;


architecture behavioral of shift_register_asis is
    signal r_reg: std_logic_vector(7 downto 0);
    signal r_next: std_logic_vector(7 downto 0);
begin
    process(clk,reset)
    begin
        if(reset = '1') then
            r_reg <= (others => '0');
        elsif (clk' event and clk = '1') then
            r_reg <= r_next;
        end if;
    end process;
    -- next state logic;
    r_next <= d & r_reg(7 downto 1);
    -- output logic
    q <= r_reg(0);
end behavioral;

```

```

-- Shift_register_siso_tb
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity shift_register_siso_tb is
-- Port ( );
end shift_register_siso_tb;
architecture Behavioral of shift_register_siso_tb is
signal reset_sig,d_sig,q_sig: std_logic;
signal clk_sig: std_logic := '0';
constant period: time := 10ns;
component shift_register_siso is
    port(      clk, reset,d : IN STD_LOGIC;
           q: OUT STD_LOGIC);
END component shift_register_siso;
begin
 uut: shift_register_siso
    port map(clk => clk_sig, reset => reset_sig,d => d_sig, q =>
q_sig);
clock: process
    begin
        clk_sig <= not clk_sig;
        wait for period/2;
    end process;
stim: process
    begin
        d_sig <= '0';
        wait for period/2;
        d_sig <= '1';
        wait for period;
        d_sig <= '0';
        wait for period;
        d_sig <= '1';
        wait for period;
        d_sig <= '1';
        wait for period;
        d_sig <= '0';
        wait for period;
        d_sig <= '1';
        wait for period;
        d_sig <= '0';
        wait;
    end process;
end Behavioral;
Shift register Results

```

 

The simulation for the shift register is easily verifiable as the input of d\_sig is shifted out after 8 cycles.

---

```
-- dff.vhd
-- simple d flip flop to hold the carry
-- Ridge Tejuco
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity dff is
    port(d,clk,reset: in std_logic;
         q: out std_logic);
end dff;
architecture Behavioral of dff is
begin
    process(clk,reset)
    begin
        if( reset = '1') then
            q <= '0';
        elsif (clk' event and clk = '1') then
            q <= d;
        end if;
    end process;
end Behavioral;
```




```

--dff_tb.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity dff_tb is
--  Port ( );
end dff_tb;
architecture Behavioral of dff_tb is
signal d_sig,reset_sig,q_sig: std_logic;
signal clk_sig: std_logic := '0';
constant period: time := 10ns;
component dff is
    port(d,clk,reset: in std_logic;
        q: out std_logic);
end component;
begin
    uut: dff
    port map(d => d_sig, clk => clk_sig, reset => reset_sig, q =>
q_sig);
    clock: process
    begin
        clk_sig <= not clk_sig;
        wait for period/2;
    end process;
    stim: process
    begin
        d_sig <= '0';
        wait for period;
        d_sig <= '1';
        wait for period/2;
        d_sig <= '0'; -- 0 should be skipped
        wait for period/2;
        d_sig <= '1';
        wait for period;
        d_sig <= '0';
        wait;
    end process;
end Behavioral;

```

## DFF results

 

The results for the d flip flop is easy to verify.

The output for q follows the input of d only when the clock is rising edge.

For example q\_sig is not set to 0 at 15ns while clk is falling.

---

```
-- Module Name: FullAdder
-- Ridge Tejuco
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FullAdder is
    Port ( cin,a,b : in STD_LOGIC;
          sum,cout : out STD_LOGIC);
end FullAdder;

architecture Behavioral of FullAdder is

begin
    cout <= (a and b) or (a and cin) or (b and cin);
    sum <= (a xor b xor cin);
end Behavioral;

-- Full Adder Testbench
```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity FullAdderTestBench is
end FullAdderTestBench;
architecture Behavioral of FullAdderTestBench is
signal cin_sig, a_sig,b_sig,cout_sig,sum_sig: STD_LOGIC;
component FullAdder is
    Port ( cin,a,b : in STD_LOGIC;
          sum,cout : out STD_LOGIC;
end component;
begin
UUT: FullAdder
port map (a => a_sig, b => b_sig,cin => cin_sig, cout => cout_sig,sum
=> sum_sig);
STIM: process
begin
    cin_sig <= '0';b_sig <= '0';a_sig <= '0';wait for 10ns;
    cin_sig <= '0';b_sig <= '0';a_sig <= '1';wait for 10ns;
    cin_sig <= '0';b_sig <= '1';a_sig <= '0';wait for 10ns;
    cin_sig <= '0';b_sig <= '1';a_sig <= '1';wait for 10ns;
    cin_sig <= '1';b_sig <= '0';a_sig <= '0';wait for 10ns;
    cin_sig <= '1';b_sig <= '0';a_sig <= '1';wait for 10ns;
    cin_sig <= '1';b_sig <= '1';a_sig <= '0';wait for 10ns;
    cin_sig <= '1';b_sig <= '1';a_sig <= '1';
    wait;
end process;
end Behavioral;

```

**Full adder** is the same as computer assignment 1

