

# Monostable Multivibrators

Ridge Tejuco, Oscar Tejada

**Abstract**—In this lab, two pulse generation circuits were designed. The resistor and capacitor values were selected to get a desired pulse width. One of the circuits built was the Op Amp Pulse Generator, which requires an op amp, diodes, resistors and capacitors. The other circuit was the 555 Timer-Based Pulse Generator, which includes a 555-timer integrated circuit, a resistor, and a capacitor. The Op Amp Pulse Generator needs to create a pulse with a 100  $\mu$ s width. The 555 Timer-Based Pulse Generator needs to create a pulse with a width of 1 ms. A high valued resistor was added to the output of the circuit as well. Different formulas were used to help find the different component values for both circuits. The pulse width was found by subtracting two points from the result plot. PSpice was used to simulate both circuits and the Op Amp Pulse Generator circuit was experimentally created on a breadboard.

## I. INTRODUCTION

The purpose of this lab is to use and understand the theory behind monostable multivibrator pulse generators. Occasionally, in the design of a circuit, a pulse of a certain amplitude and length is desired. The pulses provided by this circuit are controlled by choosing resistor values and capacitance values tied to the inverting input of the op amp. The monostable multivibrator used in this lab is an augmented circuit of the astable multivibrator used in the previous lab. In connection to the circuit, a few concepts must be understood, such as op amps, voltage dividers, RC circuits, and diodes. Additionally, the lab also introduces the use of 555 timers, one of the most popular IC's. The 555 timers can be used to implement a monostable multivibrator to produce pulses that may be desired in the design of any project. The 555 timer also includes the use of an internal RS flip flop and BJT.

## II. CIRCUIT THEORY

Looking at figure 1, it can be seen that the monostable multivibrator is an augmented circuit of the astable multivibrator. A trigger circuit composed of capacitor  $C_2$ , diode  $D_2$ , and resistor  $R_4$  was added to the non-inverting input and the

diode  $D_1$  was added to the inverting input. Unlike the astable multivibrator, the monostable multivibrator has a stable state in which it will stay in unless triggered.

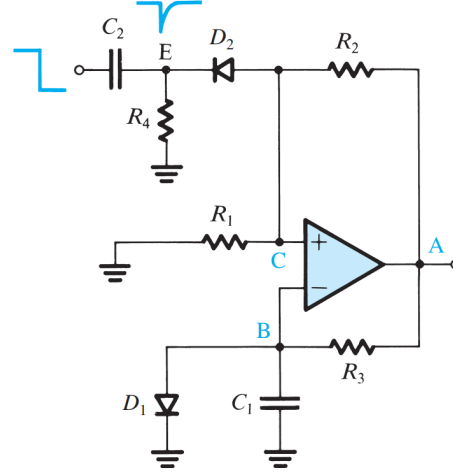


Fig. 1. The monostable multivibrator circuit.

The voltage  $V_A$  is saturated at  $L_+$ , the supply voltage of the op amp as seen in (1). This remains true until the circuit is triggered as seen in figure 2. The voltage  $V_C$  is determined by the voltage divider  $R_2$  and  $R_1$  shown in (2). Choosing  $R_4$  to be largely greater than  $R_1$  is important so that the current flowing through  $D_2$  is small.  $V_E$  will always be at a difference of  $V_{D2}$  from  $V_C$  unless triggered and eventually  $C_2$  is recharged as seen in figure 2 and (3). The voltage  $V_B$  is clamped by the diode in (4) and is discharged when the circuit is triggered as seen in figure 2. The following (1), (2), (3) and (4) show the node voltages prior to the trigger.

$$V_A = L_+ \quad (1)$$

$$V_C = \beta L_+ \quad (2)$$

$$V_E = \beta L_+ - V_{D2} \quad (3)$$

$$V_B = V_{D1} \quad (4)$$

Looking closely at figure 2, the resulting trigger from  $V_E$  also causes a dip in  $V_C$ . The difference between  $V_C$  and  $V_B$  forces  $V_A$  to drop to  $L_-$ . The negative voltage of  $V_A$  feeds back to C and sets  $V_C = \beta L_-$ . The negative voltage at A also causes the  $C_1$  to discharge as current flows the opposite way and  $D_1$  turns off. When  $V_B = V_C = \beta L_-$  the difference between  $V_B$  and  $V_C$  is 0 and  $V_A$  returns to  $L_+$ .

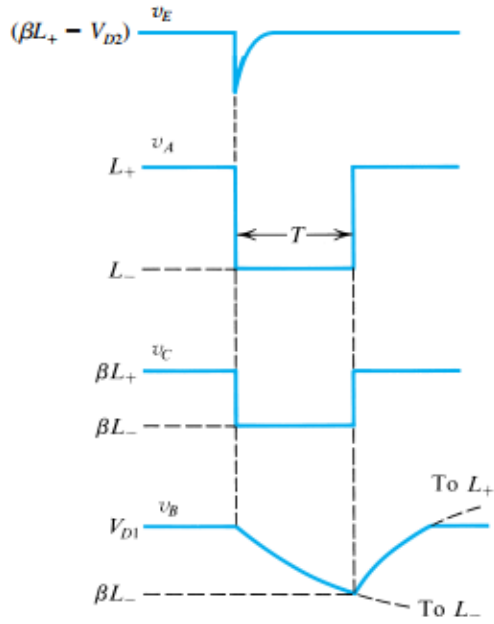


Fig. 2. Resulting node voltages of the monostable multivibrator from the trigger.

From figure 2,  $V_B$  shows that the period  $T$  of the pulse is determined by the RC time constant composed of  $C_1$  and  $R_3$ . The equation for  $V_B(t)$  is given by (5). Substituting  $t = T$  gives (6). Solving for period  $T$  results in (7). Choosing  $V_{D1}$  to be largely smaller than  $L_-$  the equation is simplified in (8).

$$V_B(t) = L_- - (L_- - V_{D1}) e^{-\frac{t}{R_3 C_1}} \quad (5)$$

$$\beta L_- = L_- - (L_- - V_{D1}) e^{-\frac{T}{R_3 C_1}} \quad (6)$$

$$T = C_1 R_3 \ln\left(\frac{V_{D1} - L_-}{\beta L_- - L_-}\right) \quad (7)$$

$$T = C_1 R_3 \ln\left(\frac{1}{1-\beta}\right) \quad (8)$$

The 555 timer IC can also be used to generate pulses of a desired width and height. Figure 3 shows the internals and implementation of the monostable multivibrator. An RC circuit is attached to the comparator 1 non-inverting input and the  $Q_1$  BJT collector.

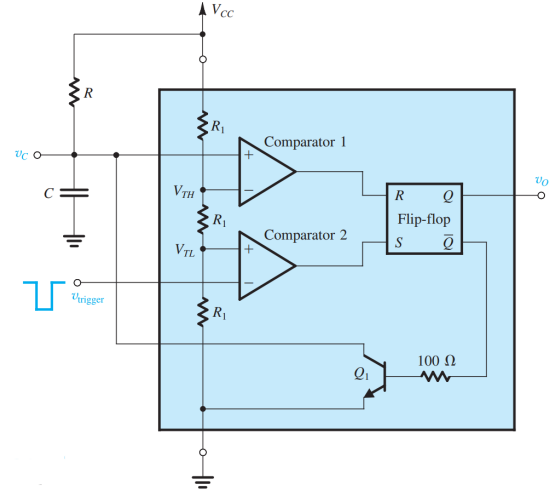


Fig. 3. The implementation of a monostable multivibrator using a 555 timer.

Initially, the 555 timer is in the steady state with the RS flip flop in its reset state. The  $Q'$  output is high and powering the  $Q_1$  transistor. Since the current is saturated through  $Q_1$ , the voltage  $V_C$  will be constantly low because no current is charging the capacitor  $C$ . With a 0 input for comparator 1 and a high input for comparator 2, the 555 timer will remain in its steady state.

The 555 timer is triggered by inputting a signal lower than  $V_{TL}$ . Once triggered, comparator 2's output goes high and the RS flip flop is set.  $V_o$  is now output high. The  $Q'$  low output turns off  $Q_1$  and the current can now start charging the capacitor  $C$ . Once capacitor  $C$ , reaches  $V_{TH}$ , comparator 1's output is set high and the RS flipflop is reset.  $V_o$  is back to output low and 555 timer is back in steady state. The process of this pulse is further illustrated in figure 4.



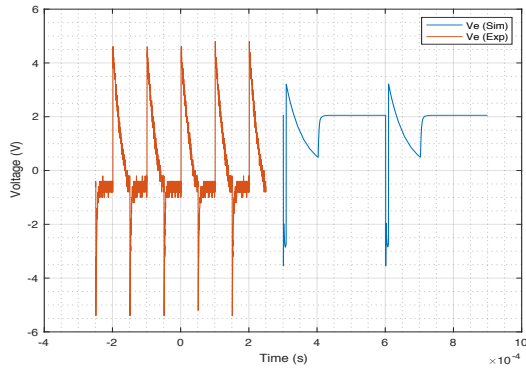


Fig. 6. Different outputs for the Op Amp Pulse Generator

The pulse width can be seen to be about 100  $\mu$ s for both simulation and experimental. The values for the 555-Timer Based Pulse Generator were  $R = 9.1 \text{ k}\Omega$  and  $C = 0.1 \text{ }\mu\text{F}$ . The circuit can be seen in Fig. 7.

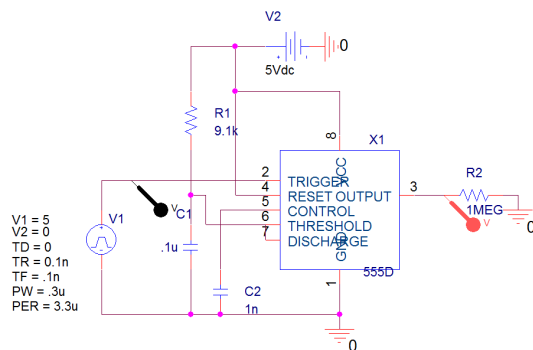


Fig. 7. 555-Timer Based Pulse Generator circuit

The output for the 555-Timer Based Pulse Generator can be seen in Fig. 8.

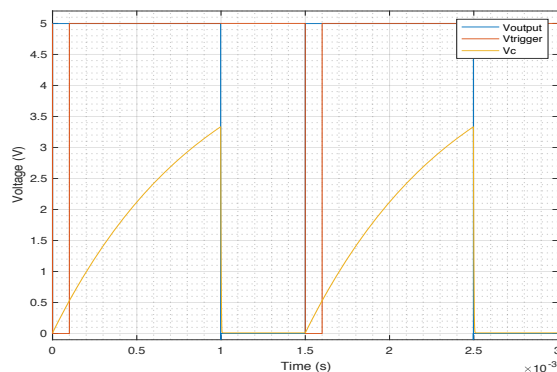


Fig. 8. 555-Timer Based Pulse Generator outputs

The pulse width measured for the output is about 1 ms.

## IV. DISCUSSION AND CONCLUSION

An op amp and diodes were used to create an Op Amp Pulse Generator. The resistors and capacitors were chosen to receive a pulse width of 100  $\mu$ s. The simulation output was 100  $\mu$ s while the experimental was about 98  $\mu$ s. A 555-Timer Based Pulse Generator was also created and the desired pulse width was 1 ms. The pulse width received was about 0.7 ms. There was no experimental value for the 555-Timer Based Pulse Generator due to campus being closed.

The experimental and simulation values were different for the Op Amp Pulse Generator due to error. One error was that the circuit was measured during different time intervals. This wasn't allowed get fixed due to the campus closure. Another error can be due to our measuring probes quality. This can account for the spikes in some of our experimental data. The voltage values aren't the same because some voltage could've been lost in the circuit.

## ACKNOWLEDGMENT

Ridge- 50% Lab, Introduction and Circuit Theory

Oscar- 50% Lab, Abstract, Simulation Results and Conclusion

## REFERENCES

- [1] Jackson, Bradley. "Monostable Multivibrators" 5 Mar. 2020, Northridge
- [2] "Monostable Multivibrator – The One-Shot Monostable." *Basic Electronics Turorials*, 4 Mar. 2018, [www.electronicstutorials.ws/waveforms/monostable.html](http://www.electronicstutorials.ws/waveforms/monostable.html).
- [3] ECE 443 Lab Manual