FPGA Features, Clock Management, DSP Blocks, DDR, and SRL

Ridge Tejuco
California State University Northridge
Department of Electrical and Computer Engineering
Northridge, California
Ridge. Tejuco.881@my.csun.edu

I. INTRODUCTION

The purpose of this experiment is to become familiar with the various features and resources found on the ZedBoard. These features include the digital clock managers, DSP blocks, and SRL and block ram configurations. The circuit used for this experiment is a multiply accumulate circuit which takes two data streams as inputs and multiplies them by given constants. The two data streams are then mixed.

The multiply accumulate circuit is implemented in three different ways, each using different FPGA resources. The first is a direct implementation of the circuit using DSP blocks. Each data stream is a sine wave, and the coefficients are values ranging from 0 to 1. The second way is an interleaver circuit which is an optimized implementation that includes clocks at each stage of the multiply accumulate circuit and multiplexers for each data stream. This implementation reduces the amount of resources needed for the operation, increases the output rate, and increases the functionality of the design. The last implementation incorporates equalizing delay. Shift right logical elements are placed at the inputs to synchronize the data streams.

II. PROCEDURE AND RESULTS

 


Fig. 3.1 Multiply Accumulate block diagram

Fig. 3.1 shows the high level block diagram of the design. Data streams P_0 and P_1 are sine waves, and alpha is a coefficient between 0 and 1. These inputs are represented by 8 bit values. The output P_f is 17 bits.

 


Fig. 3.2 Multiplier test bench results

 


Fig. 3.3 Adder test bench results

Fig 3.2 and Fig 3.3 show the results of the test benches for the multipliers and adders. The waveforms show the inputs and outputs in decimal format. Going through each results shows the correct operation of each element.

 


Fig 3.4 Multiply accumulate test bench waveform with a sine wave at signal a

Looking closely at Fig 3.4, the results of the MAC block can be seen. Signal a was a sine wave with a range of values

from 0 to 255. In this case, 0 represents a value of -1 in the sine wave and 255 represents a value of 1. For simplification, signal b was kept at a constant 0, and has no contribution to the output. For the first 80 ns, the coefficient is 127 so about half of signal a and b are added. From 80 ns to 160 ns, the coefficient is 63 so about 25% of signal a is seen at the output. Lastly from 160 ns to 200 ns, only about 5% of signal a is seen.

Fig 3.5 is given to show the reverse input where signal a is set to a value of 0, and signal b is a sine wave. For the first 80 ns, still about 50% of the sine wave is output. From 80 to 160 ns, about 75% of the sine wave is seen at the output. Then for the last 40 ns, about 95% of the sine wave can be seen at the output. These results prove the functionality of the MAC block.

 


Fig 3.5 Reversed multiply Accumulate testbench waveform with a sine wave at signal b

1. Slice Logic

+				+		+		+-		+
i	Site Type	Us	ed	i	Fixed	İ	Available	i	Util%	İ
Ī		1		÷	0	Ċ			0.30	
-	LUT as Logic	1	57	I	0	I	53200	l	0.30	I
1	LUT as Memory		0	1	0	Ī	17400	Ī	0.00	ī

Fig 3.6 Resource utilization report showing slice logic

Fig 3.6 shows a snippet from the utilization report. 157 LUTs were used meaning that Slice logic was used rather than the DSP blocks. In order to force an implementation of DSP blocks, the "use_dsp" attribute can be set. For this implementation, the use_dsp attribute could not result in forcing the use of DSP blocks.

The next implementation incorporates clocked inputs and outputs at each stage. Fig 3.7 shows the block diagram for the implementation. The multiplexers alternate between inputs and the mode of operation for new data and for accumulating the previous data stream.

 


Fig. 3.7 High performance multiply accumulator design

Fig. 3.8 shows the results of the high performance interleaver circuit design. The stimulus in the testbench for the first implementation was reused. Looking closely at the output, the output waveform is identical to the output waveform in Fig 3.4. This shows that the functionality of the first two implementations are the same.

 


Fig. 3.8 Output waveforms of interleaver design

```
-- adder.vhd
-- ECE 524 Fall 2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity adder is
   Port (
        a in, b in: in std logic vector(15 downto 0);
        sum: out std_logic_vector(16 downto 0)
    );
end adder;
architecture Behavioral of adder is
begin
    sum <= std_logic_vector(unsigned("0"&a_in)+unsigned("0"&b_in));</pre>
end Behavioral;
```

```
-- adder tb.vhd
-- ECE524 FALL2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC STD.ALL;
entity adder tb is
-- Port ();
end adder tb;
architecture Behavioral of adder tb is
component adder is
    Port (
        a_in, b_in: in std_logic_vector(15 downto 0);
        sum: out std_logic_vector(16 downto 0)
    );
end component;
signal a_sig, b_sig: std_logic_vector(15 downto 0);
signal sum sig: std logic vector(16 downto 0);
constant cp: time := 10 ns;
begin
    DUT: adder
    port map(
       a in => a_sig,
        b in => b sig,
        sum => sum_sig
    );
    process
    begin
    a sig <= "0000000000000000";
    b sig <= "000000000000000";
    wait for cp;
    a sig <= "0000000000000001";</pre>
    b sig <= "0000000000000001";
    wait for cp;
    a sig <= "0000000000000010";
    b sig <= "0000000000000010";
    wait for cp;
    a sig <= "000000000000011";
    b sig <= "000000000000011";
    wait for cp;
    a_sig <= "00000000111111111";</pre>
    b sig <= "00000000111111111";
    wait for cp;
    a sig <= "100010000001111";
    b sig <= "111111111111111";
    wait for cp;
    a sig <= "111111111111111";
    b sig <= "1111111111111111";</pre>
    wait;
    end process;
end Behavioral;
```

```
-- mac.vhd
-- ECE524 FALL2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC STD.ALL;
entity mac is
    Port (
        coef, a, b: in std logic vector(7 downto 0);
        output: out std logic vector(16 downto 0)
    attribute use dsp : string;
end mac;
architecture Behavioral of mac is
    component multiplier is
            din,alpha: in std_logic_vector(7 downto 0);
            dout: out std logic vector(15 downto 0)
    end component;
    component adder is
        Port (
            a in, b in: in std logic vector(15 downto 0);
            sum: out std logic vector(16 downto 0)
        );
    end component;
    signal mult_out1, mult_out2: std_logic_vector(15 downto 0);
    signal coef not: std logic vector(7 downto 0);
    signal output sig: std logic vector(16 downto 0);
    attribute use dsp of multiplier, adder: component is "yes";
begin
    coef not <= std_logic_vector("11111111" - unsigned(coef));</pre>
    MULT1: multiplier
    port map (
        din => a, alpha => coef,
        dout => mult out1
    MULT2: multiplier
    port map(
        din => b, alpha => coef not,
        dout => mult out2
    );
    ADD: adder
    port map (
        a in => mult_out1,
        b in => mult out2,
        sum => output sig);
    output <= output sig;</pre>
end Behavioral;
```

```
-- mac tb.vhd
-- ECE524 FALL2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC STD.ALL;
entity mac tb is
-- Port ( );
end mac tb;
architecture Behavioral of mac tb is
component mac is
    Port (
        coef, a, b: in std_logic_vector(7 downto 0);
        output: out std logic vector(16 downto 0)
    );
end component;
signal coef_sig,a_sig,b_sig: std_logic_vector(7 downto 0);
signal sin_sig: unsigned( 7 downto 0);
signal output sig: std logic vector(16 downto 0);
constant cp: time := 20 ns;
begin
    DUT: mac
    port map (
        coef => coef sig,
        a => a sig,
        b \Rightarrow b \operatorname{sig}_{\bullet}
        output => output sig
    );
    SIN GEN: process
    begin
        sin sig <= to unsigned(128,8);
        wait for cp/20;
        sin sig <= to unsigned(167,8);</pre>
        wait for cp/20;
        sin sig <= to unsigned(203,8);
        wait for cp/20;
        sin sig <= to unsigned(231,8);
        wait for cp/20;
        sin sig <= to unsigned(249,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(255,8);
        wait for cp/10;
        \sin \text{ sig} \le \cot \text{ unsigned}(249,8);
        wait for cp/10;
        sin sig <= to unsigned(231,8);
        wait for cp/10;
        sin sig <= to unsigned(203,8);
        wait for cp/10;
        sin sig <= to unsigned(167,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(128,8);
        wait for cp/10;
        sin sig <= to unsigned(88,8);
        wait for cp/10;
        sin sig <= to unsigned(53,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(24,8);
        wait for cp/10;
```

```
sin sig <= to unsigned(6,8);</pre>
        wait for cp/10;
        sin_sig <= to_unsigned(0,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(6,8);</pre>
        wait for cp/10;
        sin_sig <= to_unsigned(24,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(53,8);
        wait for cp/10;
        sin sig <= to unsigned(88,8);</pre>
        wait for cp/10;
    end process;
    STIM: process
    coef_sig <= "01111111";</pre>
    wait for 4*cp;
    coef sig <= "00111111";</pre>
    wait for 4*cp;
    coef sig <= "00001111";</pre>
    wait for 4*cp;
    wait;
    end process;
    b sig <= std logic vector(sin sig);</pre>
    a sig <= "00000000";
end Behavioral;
```

```
-- multiplier.vhd
-- ECE 524 Fall 2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity multiplier is
   Port (
        din,alpha: in std logic vector(7 downto 0);
        dout: out std logic vector(15 downto 0)
    );
end multiplier;
architecture Behavioral of multiplier is
signal ualpha, udin: unsigned(7 downto 0);
begin
    ualpha <= unsigned(alpha);</pre>
    udin <= unsigned(din);</pre>
    dout <= std logic vector(ualpha*udin);</pre>
end Behavioral;
```

```
-- multiplier tb.vhd
-- ECE524 FALL2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC STD.ALL;
entity multiplier tb is
-- Port ();
end multiplier tb;
architecture Behavioral of multiplier tb is
component multiplier is
    Port (
        din,alpha: in std_logic_vector(7 downto 0);
        dout: out std logic vector(15 downto 0)
    );
end component;
signal din_sig,alpha_sig: std_logic_vector(7 downto 0);
signal dout sig: std logic vector(15 downto 0);
constant cp: time := 10 ns;
begin
    DUT: multiplier
    port map( din => din sig,
        alpha => alpha sig,
        dout => dout sig
    );
    process
    begin
        din sig <= "00000000";
        alpha sig <= "00000000";
        wait for cp;
        din_sig <= "00000001";
        alpha sig <= "00000001";
        wait for cp;
        din sig <= "00000010";
        alpha sig <= "00000010";
        wait for cp;
        din sig <= "00000011";
        alpha sig <= "00000011";
        wait for cp;
        din sig <= "00000100";
        alpha_sig <= "00000100";
        wait for cp;
        din sig <= "00010100";
        alpha sig <= "00010100";
        wait for cp;
        din sig <= "01000000";
        alpha sig <= "11110000";
        wait for cp;
        din sig <= "111111111";</pre>
        alpha sig <= "111111111";</pre>
        wait;
    end process;
end Behavioral;
```

```
-- opt mac.vhd
-- ECE524 FALL2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC STD.ALL;
entity opt mac is
    Port (
        s0,s1,coeff: in std logic vector(7 downto 0);
        clk, clk2, clkhalf: in std logic;
        Blend: out std logic vector(16 downto 0)
end opt mac;
architecture Behavioral of opt mac is
component multiplier is
        din,alpha: in std_logic_vector(7 downto 0);
        dout: out std logic vector(15 downto 0)
    );
end component;
component adder is
    Port (
        a in, b in: in std logic vector(15 downto 0);
        sum: out std logic vector(16 downto 0)
end component;
signal s_in,s0_buf,s1_buf: std_logic_vector(7 downto 0);
signal alpha buf, alpha bufnot, alpha in: std logic vector(7 downto 0);
signal mult out: std logic vector(15 downto 0);
signal add in: std logic vector(15 downto 0);
signal add out, sum buf: std logic vector(16 downto 0);
begin
    MULT: multiplier
    port map(
        din => s_in,
        alpha => alpha in,
        dout => mult out
    );
    ADD: adder
    port map (
        a in => mult out,
        b in => add in,
        sum => add out
    );
    process(clk)
    begin
        if(rising_edge(clk)) then
            s1 buf <= s1;
            s0 buf <= s0;
            alpha buf <= coeff;
            alpha_bufnot <= std_logic_vector("11111111"-unsigned(coeff));</pre>
            Blend <= sum buf;</pre>
        end if;
    end process;
    process(clk2)
    begin
        if rising edge(clk2) then
            sum buf <= add out;</pre>
```

```
end if;
end process;

process(clkhalf)
begin
if(clkhalf = '0')then
   add_in <= (others => '0');
   alpha_in <= alpha_buf;
   s_in <= s0_buf;
else
   add_in <= sum_buf(15 downto 0);
   alpha_in <= alpha_bufnot;
   s_in <= s1_buf;
end if;
end process;
end Behavioral;</pre>
```

```
-- opt mac tb.vhd
-- ECE524 FALL2020
-- Ridge Tejuco
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity opt mac tb is
-- Port ( );
end opt mac tb;
architecture Behavioral of opt mac tb is
component opt mac is
    Port (
        s0,s1,coeff: in std_logic_vector(7 downto 0);
        clk,clk2,clkhalf: in std logic;
        Blend: out std logic vector(16 downto 0)
end component;
signal s0 sig, s1 sig, coef sig: std logic vector(7 downto 0);
signal sin sig: unsigned(7 downto 0);
signal clk_sig,clk2_sig,clkhalf_sig: std_logic := '0';
signal Blend sig: std logic vector(16 downto 0);
constant cp: time := \overline{40} ns;
begin
    DUT: opt mac
    port map (
        s0 \Rightarrow s0 siq
        s1 => s1_sig,
        coeff => coef sig,
        clk => clk sig,
        clk2 => clk2 siq
        clkhalf => clkhalf sig,
        Blend => Blend sig
    );
    CLK: process(clk sig)
        clk sig <= not clk sig after cp/20;
    end process;
    CLK2: process(clk2 sig)
    begin
    clk2 sig <= not clk2 sig after cp/40;
    end process;
    MODE GEN: process(clkhalf sig)
    begin
    clkhalf sig <= not clkhalf sig after cp/10;</pre>
    end process;
    STIM: process
    begin
    coef sig <= "01111111";</pre>
    wait for 4*cp;
    coef sig <= "001111111";</pre>
    wait for 4*cp;
    coef_sig <= "00001111";</pre>
    wait for 4*cp;
    wait;
    end process;
```

```
SIN GEN: process
    begin
        sin_sig <= to_unsigned(128,8);</pre>
        wait for cp/20;
        sin sig <= to unsigned(167,8);</pre>
        wait for cp/20;
        sin sig <= to unsigned(203,8);</pre>
        wait for cp/20;
        \sin \sin \ll \cot (231,8);
        wait for cp/20;
        sin sig <= to unsigned(249,8);
        wait for cp/10;
        sin_sig <= to_unsigned(255,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(249,8);</pre>
        wait for cp/10;
        sin_sig <= to_unsigned(231,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(203,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(167,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(128,8);
        wait for cp/10;
        sin sig <= to unsigned(88,8);
        wait for cp/10;
        sin_sig <= to_unsigned(53,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(24,8);
        wait for cp/10;
        sin sig <= to unsigned(6,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(0,8);
        wait for cp/10;
        sin_sig <= to_unsigned(6,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(24,8);
        wait for cp/10;
        sin sig <= to unsigned(53,8);</pre>
        wait for cp/10;
        sin sig <= to unsigned(88,8);
        wait for cp/10;
    end process;
    s0 sig <= std logic vector(sin sig);</pre>
    s1 sig <= "00000000";
end Behavioral;
```