

EXPLORING XILINX VIVADO IDE AND ZEDBOARD

Ridge Tejuco

California State University, Northridge, Electrical and Computer Engineering Department
ridge.tejuco.881@my.csun.edu

Abstract:

The Zedboard is an fpga development board using the Xilinx Zynq-7000 SoC. The Zedboard provides a wide range of functions and interfaces that enable developers to rapidly prototype circuit designs. This experiment covers the design and implementation of a logical circuit onto a Zedboard. The design consists of 8 LEDs controlled by various types of 8 bit counters. The circuit was coded in VHDL and simulated in Vivado. Various test benches were constructed resulting in the expected sequences for each counter. Due to restrictions in place for Covid-19, the physical lab and Zedboard is unavailable and only the simulation and VHDL code is included in the report.

Keywords:

Vivado, BCD, Gray Code, Johnson, Fibonacci, Zedboard, Binary Counter, Ring Counter, VHDL

1.1 INTRODUCTION

The purpose of this experiment is to become familiar with the Vivado IDE and Zedboard. The experiment consists of building an LED circuit controlled by 6 different counters. Fig. 1.1 shows the top level block diagram for the counter design. The 6 different counters include Binary, Gray Code, BCD, Ring, Johnson and Fibonacci counters. Each counter is connected to a multiplexer that is passed through to the LEDs. In order to visualize the physical changes in the 8 LEDs, a frequency divider is used to divide the onboard clock of 100 MHz.

 


Fig. 1.1 General counter diagram with clock divider

In order to access the Onboard clock, switches, and LED pins, a constraint file must be included with the project. The constraint file for the Zedboard was downloaded from the Zedboard documentation webpage and imported to the project. In the XDC file, the pins and interfaces are directly mapped to the ports of the modules defined in the project. Fig 1.2 shows the Zedboard constraint file and an example of how the LED ports should be connected to the top module ports can be seen in Fig 1.3. The constraint file is included in the Appendix, but since the Zedboard is unavailable, the constraint file is not required for the simulation.

 


Fig. 1.2 The zedboard constraint file shown within the project hierarchy

```
# Design Constraint File

# -----
# Clock Source - Bank 13
# -----
set_property PACKAGE_PIN Y9 [get_ports {OnboardClock}]; # "GCLK"

# -----
# User LEDs - Bank 33
# -----

set_property PACKAGE_PIN T22 [get_ports {LedOut[0]}]; # "LD0"
set_property PACKAGE_PIN T21 [get_ports {LedOut[1]}]; # "LD1"
set_property PACKAGE_PIN U22 [get_ports {LedOut[2]}]; # "LD2"
set_property PACKAGE_PIN U21 [get_ports {LedOut[3]}]; # "LD3"
set_property PACKAGE_PIN V22 [get_ports {LedOut[4]}]; # "LD4"
set_property PACKAGE_PIN W22 [get_ports {LedOut[5]}]; # "LD5"
set_property PACKAGE_PIN U19 [get_ports {LedOut[6]}]; # "LD6"
set_property PACKAGE_PIN U14 [get_ports {LedOut[7]}]; # "LD7"

# -----
# User DIP Switches - Bank 35
# -----

set_property PACKAGE_PIN F22 [get_ports {select_top[0]}]; # "SW0"
set_property PACKAGE_PIN G22 [get_ports {select_top[1]}]; # "SW1"
set_property PACKAGE_PIN H22 [get_ports {select_top[2]}]; # "SW2"
```

Fig. 1.3 The constraint file code for access to the LEDs, Onboard clock, and switches.

To find information about the design's utilization of FPGA resources, the design is synthesized. After the synthesis is done, a synthesis report file is created. The slice logic section within the report is shown in Fig 1.4

```

27 1. Slice Logic
28 -----
29
30 +-----+-----+-----+-----+-----+
31 | Site Type | Used | Fixed | Available | Util% |
32 +-----+-----+-----+-----+-----+
33 | Slice LUTs* | 74 | 0 | 53200 | 0.14 |
34 | LUT as Logic | 74 | 0 | 53200 | 0.14 |
35 | LUT as Memory | 0 | 0 | 17400 | 0.00 |
36 | Slice Registers | 49 | 0 | 106400 | 0.05 |
37 | Register as Flip Flop | 49 | 0 | 106400 | 0.05 |
38 | Register as Latch | 0 | 0 | 106400 | 0.00 |
39 | F7 Muxes | 0 | 0 | 26600 | 0.00 |
40 | F8 Muxes | 0 | 0 | 13300 | 0.00 |
41 +-----+-----+-----+-----+-----+

```

Fig. 1.4 LUT and Flip Flop utilization details in the design synthesis report

In order to program the FPGA, the design must be implemented and then a bitstream must be generated. The bitstream file is located in the project folder, usually within the “/projectName.runs/impl_1” folder.

1.2 PROCEDURE AND RESULTS

The input clock frequency is 100 MHz. A clock frequency of 1 Hz is required to see the physical light changes in the LED. The following (1) shows the required number of bits for the frequency divider in order to achieve 1 Hz. A frequency of 1 Hz drastically increases the simulation time required, therefore, for the sake of simulation, the frequency divider was reduced to 1 bit and a frequency of 50 MHz was used for the final simulations. Fig 1.5 shows the results of the frequency divider testbench that was run for 1.4 s. Looking closely, a pulse can be seen at around 1.34 s. This is the expected period for a frequency of 0.745 Hz.

$$\frac{100 * 1000 * 1000 \text{ Hz}}{2^{27}} = 0.74505 \text{ Hz} \quad (1)$$

 


Fig. 1.5 The clock signal of about 1 Hz in simulation

6 different counters were designed in this experiment. This includes a binary, bcd, gray counter, johnson, ring, and a fibonacci counter. Fig 1.6 shows the simulation

results of all 6 counters. Each result shows the expected sequence when for each type of counter. In Fig 1.6, the counters all pause when the pause signal is set to '1'. In Fig 1.7, the counters begin their sequences in reverse as the direction signal is set to '0'.

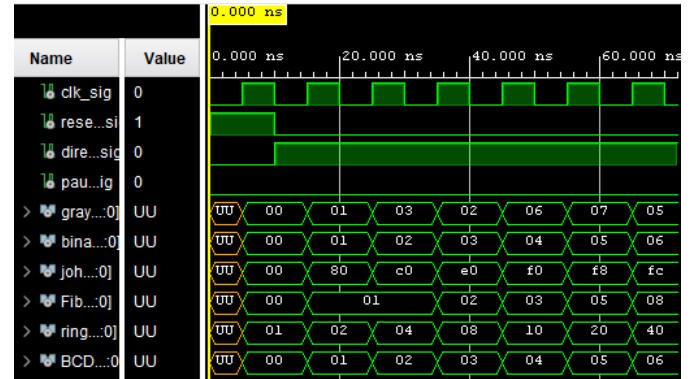


Fig 1.6 Simulation results of all 6 counters counting upwards

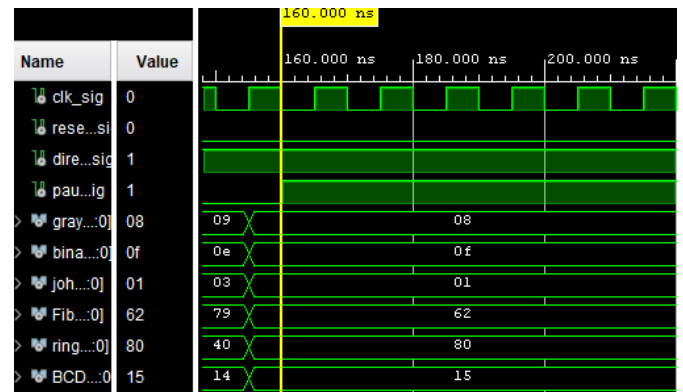


Fig 1.7 Simulation results of all 6 counters during a pause

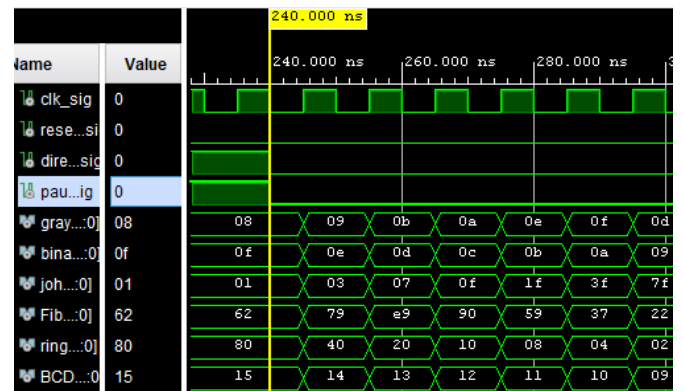


Fig 1.8 Simulation results of all 6 counters counting down

The last component of the overall design was the multiplexer. The multiplexer has a select line of 3 bits, each combination representing a type of counter. Fig 1.9 shows the simulation results of the multiplexer. For the sake of simplicity in testing, the types of counters are represented by one-hot code rather than an actual implementation of the counters. For example, binary is represented as “00000001” , a ring counter is represented as “00000010”, and johnson counter is represented as “00000100” and so on.



Fig 1.9 Simulation results of the multiplexer design

Fig 1.10 through Fig. 1.12 show the simulation results for the binary counter in the top level design with select set to 0. After the binary counter, the simulation continues from here to show each counter with the same inputs. Each different select showed the same pattern of counting up within their respective sequences and then counting backwards. While not exhaustive ,this test bench was a good indication that the design and implementation was correct.

 


Fig 1.10 Simulation of the top level counter design for binary counting up

 


Fig 1.11 Simulation of the top level counter design for binary during pause

 


Fig 1.12 Simulation of the top level counter design for binary counting down

1.3. DISCUSSION AND CONCLUSION:

Overall the experiment was a success in implementation of this top level counter onto the Zedboard. The simulation results show the correct sequences for all 6 counters in our top level design. Unfortunately, the Zedboards are not available this semester for physical testing and implementation of the VHDL code; However, the file configurations for the Zedboard were properly set up, and the project was able to be synthesized and implemented.

REFERENCES

[1]<http://www.ecs.csun.edu/~smirzaei/docs/ece524/ece524fall20-lab1-exploring-vivado-ide.pdf>
[2]<http://zedboard.org/sites/default/files/documentations/GS-AES-Z7EV-7Z020-G-V7-1.pdf>
[3]<https://www.ics.uci.edu/~jmoorkan/vhdlref/Synario%20VHDL%20Manual.pdf>

```

-- LedCounterTop.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity LedCounterTop is
    Port(
        OnboardClock, pause_top, reset_top,divider_reset, direction_top: in std_logic;
        select_top: in std_logic_vector(2 downto 0);
        LedOut: out std_logic_vector (7 downto 0)
    );
end LedCounterTop;

architecture Behavioral of LedCounterTop is
    component FrequencyDivider is
        port(
            clk,reset:in std_logic;
            DOUT: out std_logic
        );
    end component;

    component GrayCounter is
        port(
            gray_clk,gray_reset,gray_direction,gray_pause:in std_logic;
            gray_DOUT: out std_logic_vector(7 downto 0);
            binary_DOUT: out std_logic_vector(7 downto 0)
        );
    end component;

    component RingCounter is
        port(
            clk,reset,direction,pause:in std_logic;
            DOUT: out std_logic_vector(7 downto 0)
        );
    end component;

    component JohnsonCounter is
        port(
            clk,reset,direction,pause:in std_logic;
            DOUT: out std_logic_vector(7 downto 0)
        );
    end component;

    component BCDCounter is
        port(
            clk,reset,direction,pause:in std_logic;
            DOUT: out std_logic_vector(7 downto 0)
        );
    end component;

-- LedCounterTop.vhd Continued
end component;

```

```

component FibCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end component;

component CounterMultiplexer is
    Port (
        counter_select: in std_logic_vector(2 downto 0);
        FibIn,GrayIn,BinIn,BCDIn,JohnIn,RingIn: in std_logic_vector(7 downto 0);
        LED: out std_logic_vector(7 downto 0)
    );
end component;

signal oneHz: std_logic;
signal BinMuxIn, RingMuxIn, JohnMuxIn: std_logic_vector(7 downto 0);
signal GrayMuxIn, BCDMuxIn, FibMuxIn : std_logic_vector(7 downto 0);
signal pause_sig, reset_sig, direction_sig: std_logic;
signal select_sig: std_logic_vector(2 downto 0);
signal OutSig: std_logic_vector(7 downto 0);

begin
    pause_sig <= pause_top;
    reset_sig <= reset_top;
    direction_sig <= direction_top;
    select_sig <= select_top;
    FreqDiv: FrequencyDivider
    port map(
        clk => OnboardClock,
        reset => divider_reset,
        DOUT => oneHz
    );

    BinGrayCntr: GrayCounter
    port map(
        gray_clk => oneHz, gray_reset => reset_sig,
        gray_direction => direction_sig, gray_pause => pause_sig,
        gray_DOUT => GrayMuxIn, binary_DOUT => BinMuxIn
    );

    RingCntr: RingCounter
    port map(
        clk => oneHz, reset => reset_sig,
        direction => direction_sig, pause => pause_sig,
        -- LedCounterTop.vhd Continued
        DOUT => RingMuxIn
    );

    JohnCntr: JohnsonCounter
    port map(
        clk => oneHz, reset => reset_sig,

```

```

        direction => direction_sig, pause => pause_sig,
        DOUT => JohnMuxIn
    );

BCDCntr: BCDCounter
port map(
    clk => oneHz, reset => reset_sig,
    direction => direction_sig, pause => pause_sig,
    DOUT => BCDMuxIn
);

FibCntr: FibCounter
port map(
    clk => oneHz, reset => reset_sig,
    direction => direction_sig, pause => pause_sig,
    DOUT => FibMuxIn
);

CntrMux: CounterMultiplexer
port map(
    counter_select => select_sig,
    FibIn => FibMuxIn, GrayIn => GrayMuxIn,
    BinIn => BinMuxIn ,BCDIn => BCDMuxIn,
    JohnIn => JohnMuxIn, RingIn => RingMuxIn,
    LED => OutSig
);
LedOut <= OutSig;
end Behavioral;
```

```

-- LedCounterTopTB.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity LedCounterTopTB is
-- Port ( );
end LedCounterTopTB;
architecture Behavioral of LedCounterTopTB is
component LedCounterTop is
    Port(
        OnboardClock, pause_top, reset_top,divider_reset, direction_top: in std_logic;
        select_top: in std_logic_vector(2 downto 0);
        LedOut: out std_logic_vector (7 downto 0)
    );
end component;
signal clock: std_logic := '0';
signal pause_sig,reset_sig,divider_reset_sig,direction_sig: std_logic;
signal LedSig: std_logic_vector(7 downto 0);
signal select_count: unsigned (2 downto 0);
constant cp: time := 10 ns;
begin
    DUT: LedCounterTop
    port map(
        OnboardClock => clock,
        pause_top => pause_sig,
        reset_top => reset_sig,
        divider_reset => divider_reset_sig,
        direction_top => direction_sig,
        select_top => std_logic_vector(select_count),
        LedOut => LedSig
    );
    clock_gen: process(clock)
    begin
        clock <= not clock after cp/2;
    end process;
    stim: process
    begin
        divider_reset_sig <= '1';
        select_count <= "000";
        pause_sig <= '0';
        direction_sig <= '1';
        wait for cp;
        divider_reset_sig <= '0';
        -- 000 Binary
        -- 001 Ring
        -- 010 John
        -- 011 Gray
-- LedCounterTopTB.vhd
-- 100 BCD
-- 101+ Fib

```

```
for ii in 0 to 5 loop
    reset_sig <= '1';
    wait for 2*cp;
    reset_sig <= '0';
    direction_sig <= '1';
    wait for 16*cp;
    pause_sig <= '1';
    wait for 8*cp;
    pause_sig <= '0';
    direction_sig <= '0';
    wait for 24*cp;
    select_count <= select_count + 1;
end loop;
wait;
end process;
end Behavioral;
```



```

--FrequencyDivider.vhd
library ieee;
use ieee.numeric_std.all;
use ieee.std_logic_1164.all;
use ieee.std_logic_misc.all;
entity FrequencyDivider is
    port(
        clk,reset:in std_logic;
        DOUT: out std_logic
    );
end FrequencyDivider;
architecture behavioral of FrequencyDivider is
    signal count: unsigned(0 downto 0);
begin
    process(clk)
    begin
        if clk = '1' and clk' event then
            if reset = '1' then
                count <= (others => '0');
            else
                count <= count + 1;
            end if;
        end if;
    end process;
    DOUT <= and_reduce(std_logic_vector(count));
end architecture;

```

```

-- FrequencyDividerTB.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity FrequencyDividerTB is
-- Port ( );
end FrequencyDividerTB;

architecture Behavioral of FrequencyDividerTB is
component FrequencyDivider is
    port(
        clk,reset:in std_logic;
        DOUT: out std_logic
    );
end component;
signal clk_sig, reset_sig: std_logic := '0';
signal DOUT_sig: std_logic;
constant cp: time := 10 ns;
begin
    DUT: FrequencyDivider
    port map(
        clk => clk_sig,
        reset => reset_sig,
        DOUT => DOUT_sig
    );
    clock_gen:process(clk_sig)
    begin
        clk_sig <= not clk_sig after cp/2;
    end process;

    stim: process
    begin
        reset_sig <= '1';
        wait for cp;
        reset_sig <= '0';
        wait;
    end process;
end Behavioral;

```

```

--GrayBinaryCounter.vhd;
library ieee;
use ieee.numeric_std.all;
use ieee.std_logic_1164.all;
entity GrayCounter is
    port(
        gray_clk,gray_reset,gray_direction,gray_pause:in std_logic;
        gray_DOUT: out std_logic_vector(7 downto 0);
        binary_DOUT: out std_logic_vector(7 downto 0)
    );
end GrayCounter;

architecture behavioral of GrayCounter is
    component BinaryCounter is
        port(
            clk,reset,direction,pause:in std_logic;
            DOUT: out std_logic_vector(7 downto 0)
        );
    end component;
    signal BinOut: std_logic_vector(7 downto 0);
begin
    BinCntr: BinaryCounter
    port map(clk => gray_clk,reset => gray_reset,
        direction => gray_direction,
        pause => gray_pause,
        DOUT => BinOut
    );
    binary_DOUT <= BinOut;
    gray_DOUT(7) <= BinOut(7);
    gray_DOUT(6) <= BinOut(7) xor BinOut(6);
    gray_DOUT(5) <= BinOut(6) xor BinOut(5);
    gray_DOUT(4) <= BinOut(5) xor BinOut(4);
    gray_DOUT(3) <= BinOut(4) xor BinOut(3);
    gray_DOUT(2) <= BinOut(3) xor BinOut(2);
    gray_DOUT(1) <= BinOut(2) xor BinOut(1);
    gray_DOUT(0) <= BinOut(1) xor BinOut(0);
end architecture;

```

```

--RingCounter.vhd;
library ieee;
use ieee.numeric_std.all;
use ieee.std_logic_1164.all;
entity RingCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end RingCounter;

architecture behavioral of RingCounter is
    signal count: unsigned (7 downto 0);
begin
    DOUT <= std_logic_vector(count);
    process(clk)
    begin
        if clk = '1' and clk' event then
            if reset = '1' then
                count <= "00000001";
            elsif pause = '1' then
                count <= count;
            elsif direction = '0' then
                count <= count(0) & count(7 downto 1);
            else
                count <= count(6 downto 0) & count(7);
            end if;
        end if;
    end process;
end architecture;

```

```

--JohnsonCounter.vhd;
library ieee;
use ieee.numeric_std.all;
use ieee.std_logic_1164.all;
entity JohnsonCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end JohnsonCounter;

architecture behavioral of JohnsonCounter is
    signal count: unsigned (7 downto 0);
begin
    DOUT <= std_logic_vector(count);
    process(clk)
    begin
        if clk = '1' and clk' event then
            if reset = '1' then
                count <= (others => '0');
            elsif pause = '1' then
                count <= count;
            elsif direction = '1' then
                count <= (not count(0)) & count(7 downto 1);
            else
                count <= count(6 downto 0) & (not count(7));
            end if;
        end if;
    end process;
end architecture;

```

```

--BCDCounter.vhd;
library ieee;
use ieee.numeric_std.all;
use ieee.std_logic_1164.all;
entity BCDCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end BCDCounter;
architecture behavioral of BCDCounter is
    signal digit1,digit2: unsigned (3 downto 0);
begin
    process(clk)
    begin
        if clk = '1' and clk' event then
            if reset = '1' then
                digit1 <= (others => '0');
                digit2 <= (others => '0');
            elsif pause = '1' then
                digit1 <= digit1;
                digit2 <= digit2;
            elsif direction = '1' then
                if(digit1 = "1001" and digit2 = "1001")then
                    digit1 <= (others => '0');
                    digit2 <= (others => '0');
                elsif(digit1 = "1001") then
                    digit1 <= (others => '0');
                    digit2 <= digit2 + 1;
                else
                    digit1 <= digit1 + 1;
                end if;
            else
                if(digit1 = "0000" and digit2 = "0000")then
                    digit1 <= ("1001");
                    digit2 <= ("1001");
                elsif(digit1 = "0000") then
                    digit1 <= ("1001");
                    digit2 <= digit2 - 1;
                else
                    digit1 <= digit1 - 1;
                end if;
            end if;
        end process;
        DOUT <= std_logic_vector(digit2&digit1);
    end architecture;

```

```

--FibCounter.vhd;
library ieee;
use ieee.numeric_std.all;
use ieee.std_logic_1164.all;
entity FibCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end FibCounter;
architecture behavioral of FibCounter is
    signal count,temp: unsigned (7 downto 0);
begin
    DOUT <= std_logic_vector(temp);
    process(clk)
    begin
        if clk = '1' and clk' event then
            if reset = '1' then
                temp <= (others => '0');
                count <= "00000001";
            elsif pause = '1' then
                count <= count;
                temp <= temp;
            elsif direction = '1' then
                temp <= count;
                count <= count + temp;
            else
                count <= temp;
                temp <= count - temp;
            end if;
        end if;
    end process;
end architecture;

```

```

--CounterTB.vhd;
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity CounterTB is
-- Port ( );
end CounterTB;
architecture Behavioral of CounterTB is
component GrayCounter is
    port(
        gray_clk,gray_reset,gray_direction,gray_pause:in std_logic;
        gray_DOUT: out std_logic_vector(7 downto 0);
        binary_DOUT: out std_logic_vector(7 downto 0)
    );
end component;
component JohnsonCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end component;
component FibCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end component;
component RingCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end component;
component BCDCounter is
    port(
        clk,reset,direction,pause:in std_logic;
        DOUT: out std_logic_vector(7 downto 0)
    );
end component;
signal clk_sig,reset_sig,direction_sig,pause_sig: std_logic := '0';
signal gray_out_sig,binary_out_sig: std_logic_vector(7 downto 0);
signal johnson_out_sig,Fib_out_sig: std_logic_vector(7 downto 0);
signal ring_out_sig,BCD_out_sig: std_logic_vector(7 downto 0);
constant cp: time := 10 ns;
begin
    DUT0: GrayCounter
    port map(
        gray_clk => clk_sig, gray_reset => reset_sig,
        gray_direction => direction_sig,gray_pause => pause_sig,
        gray_DOUT => gray_out_sig,
        binary_DOUT => binary_out_sig
    );

```



```

);
DUT1: JohnsonCounter
port map(
clk => clk_sig, reset => reset_sig,
direction => direction_sig, pause => pause_sig,
DOOUT => johnson_out_sig
);
DUT2: FibCounter
port map(
clk => clk_sig, reset => reset_sig,
direction => direction_sig, pause => pause_sig,
DOOUT => fib_out_sig
);
DUT3: RingCounter
port map(
clk => clk_sig, reset => reset_sig,
direction => direction_sig, pause => pause_sig,
DOOUT => ring_out_sig
);
DUT4: BCDCounter
port map(
clk => clk_sig, reset => reset_sig,
direction => direction_sig, pause => pause_sig,
DOOUT => BCD_out_sig
);
clock_gen:process(clk_sig)
begin
clk_sig <= not clk_sig after cp/2;
end process;
stim: process
begin
-- pause_sig <= '0';
-- direction_sig <= '1';
reset_sig <= '1';
wait for cp;
reset_sig <= '0';
direction_sig <= '1';
wait for 15*cp;
pause_sig <= '1';
wait for 8*cp;
pause_sig <= '0';
direction_sig <= '0';
wait for 15*cp;
wait;
end process;
end Behavioral;

```

```

--CounterMultiplexer.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity CounterMultiplexer is
    Port (
        counter_select: in std_logic_vector(2 downto 0);
        FibIn,GrayIn,BinIn,BCDIn,JohnIn,RingIn: in std_logic_vector(7 downto 0);
        LED: out std_logic_vector(7 downto 0)
    );
end CounterMultiplexer;
architecture Behavioral of CounterMultiplexer is
begin
    process(counter_select,BinIn,RingIn,JohnIn,GrayIn,BCDIn,FibIn)
    begin
        case counter_select is
            when "000" => LED <= BinIn;
            when "001" => LED <= RingIn;
            when "010" => LED <= JohnIn;
            when "011" => LED <= GrayIn;
            when "100" => LED <= BCDIn;
            when others => LED <= FibIn;
        end case;
    end process;
end Behavioral;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity CounterMultiplexerTB is
-- Port ( );
end CounterMultiplexerTB;
architecture Behavioral of CounterMultiplexerTB is
component CounterMultiplexer is
    Port (
        counter_select: in std_logic_vector(2 downto 0);
        FibIn, GrayIn, BinIn,BCDIn,JohnIn,RingIn: in std_logic_vector(7 downto 0);
        LED: out std_logic_vector(7 downto 0)
    );
end component;
signal FibSig,GraySig,BinSig,BCDSig,JohnSig,RingSig: std_logic_vector(7 downto 0);
signal LEDSig: std_logic_vector(7 downto 0);
signal selCnt: unsigned (2 downto 0);
constant cp: time := 10 ns;
begin
    DUT: CounterMultiplexer
    port map(
        counter_select => std_logic_vector(selCnt),
        FibIn => FibSig,
        GrayIn => GraySig,
        BinIn => BinSig,
        BCDIn => BCDSig,
        JohnIn => JohnSig,
        RingIn => RingSig,
        LED => LEDSig
    );
    STIM: process
    begin
        BinSig <= "00000001";
        RingSig <= "00000010";
        JohnSig <= "00000100";
        GraySig <= "00001000";
        BCDSig <= "00010000";
        FibSig <= "00100000";
        -- Rather than attaching the counter modules to each signal
        -- This test bench represents each counter by a one hot value
        selCnt <= "000";
        for ii in 0 to 7 loop
            wait for cp;
            selCnt <= selCnt + 1;
        end loop;
        wait;
    end process;
end Behavioral;

```

Design Constraint File

Clock Source - Bank 13

set_property PACKAGE_PIN Y9 [get_ports {OnboardClock}]; # "GCLK"

User LEDs - Bank 33

set_property PACKAGE_PIN T22 [get_ports {LedOut[0]}}]; # "LD0"

set_property PACKAGE_PIN T21 [get_ports {LedOut[1]}}]; # "LD1"

set_property PACKAGE_PIN U22 [get_ports {LedOut[2]}}]; # "LD2"

set_property PACKAGE_PIN U21 [get_ports {LedOut[3]}}]; # "LD3"

set_property PACKAGE_PIN V22 [get_ports {LedOut[4]}}]; # "LD4"

set_property PACKAGE_PIN W22 [get_ports {LedOut[5]}}]; # "LD5"

set_property PACKAGE_PIN U19 [get_ports {LedOut[6]}}]; # "LD6"

set_property PACKAGE_PIN U14 [get_ports {LedOut[7]}}]; # "LD7"

User DIP Switches - Bank 35

set_property PACKAGE_PIN F22 [get_ports {select_top[0]}}]; # "SW0"

set_property PACKAGE_PIN G22 [get_ports {select_top[1]}}]; # "SW1"

set_property PACKAGE_PIN H22 [get_ports {select_top[2]}}]; # "SW2"

Copyright 1986-2020 Xilinx, Inc. All Rights Reserved.

```
-----
| Tool Version : Vivado v.2020.1 (win64) Build 2902540 Wed May 27 19:54:49 MDT
2020
| Date        : Tue Sep 15 21:33:54 2020
| Host        : Ridge-PC running 64-bit major release (build 9200)
| Command     : report_utilization -file LedCounterTop_utilization_synth.rpt -pb
LedCounterTop_utilization_synth.pb
| Design      : LedCounterTop
| Device      : 7z020clg484-1
| Design State : Synthesized
-----
```

Utilization Design Information

Table of Contents

-
- 1. Slice Logic
- 1.1 Summary of Registers by Type
- 2. Memory
- 3. DSP
- 4. IO and GT Specific
- 5. Clocking
- 6. Specific Feature
- 7. Primitives
- 8. Black Boxes
- 9. Instantiated Netlists

1. Slice Logic

Site Type	Used	Fixed	Available	Util%
Slice LUTs*	74	0	53200	0.14
LUT as Logic	74	0	53200	0.14
LUT as Memory	0	0	17400	0.00
Slice Registers	49	0	106400	0.05
Register as Flip Flop	49	0	106400	0.05
Register as Latch	0	0	106400	0.00
F7 Muxes	0	0	26600	0.00
F8 Muxes	0	0	13300	0.00

* Warning! The Final LUT count, after physical optimizations and full implementation, is typically lower. Run opt_design after synthesis, if not already completed, for a more realistic count.

1.1 Summary of Registers by Type

Total	Clock Enable	Synchronous	Asynchronous
0	-	-	-
0	-	-	Set
0	-	-	Reset
0	-	Set	-
0	-	Reset	-
0	Yes	-	-
0	Yes	-	Set
0	Yes	-	Reset
2	Yes	Set	-
47	Yes	Reset	-

2. Memory

Site Type	Used	Fixed	Available	Util%
Block RAM Tile	0	0	140	0.00
RAMB36/FIFO*	0	0	140	0.00
RAMB18	0	0	280	0.00

* Note: Each Block RAM Tile only has one FIFO logic available and therefore can accommodate only one FIFO36E1 or one FIFO18E1. However, if a FIFO18E1 occupies a Block RAM Tile, that tile can still accommodate a RAMB18E1

3. DSP

Site Type	Used	Fixed	Available	Util%
DSPs	0	0	220	0.00

4. IO and GT Specific

Site Type	Used	Fixed	Available	Util%
Bonded IOB	16	0	200	8.00
Bonded IPADs	0	0	2	0.00
Bonded IOPADs	0	0	130	0.00
PHY_CONTROL	0	0	4	0.00
PHASER_REF	0	0	4	0.00
OUT_FIFO	0	0	16	0.00
IN_FIFO	0	0	16	0.00
IDELAYCTRL	0	0	4	0.00
IBUFDS	0	0	192	0.00
PHASER_OUT/PHASER_OUT_PHY	0	0	16	0.00
PHASER_IN/PHASER_IN_PHY	0	0	16	0.00
IDELAYE2/IDELAYE2_FINEDELAY	0	0	200	0.00
ILOGIC	0	0	200	0.00
OLOGIC	0	0	200	0.00

5. Clocking

Site Type	Used	Fixed	Available	Util%
BUFGCTRL	2	0	32	6.25
BUFIO	0	0	16	0.00
MMCME2_ADV	0	0	4	0.00
PLLE2_ADV	0	0	4	0.00
BUFMRCE	0	0	8	0.00
BUFHCE	0	0	72	0.00
BUFR	0	0	16	0.00

6. Specific Feature

Site Type	Used	Fixed	Available	Util%
BSCANE2	0	0	4	0.00
CAPTUREE2	0	0	1	0.00
DNA_PORT	0	0	1	0.00
EFUSE_USR	0	0	1	0.00
FRAME_ECCE2	0	0	1	0.00

